

Gates and Boolean Logic


CS 3410: Computer System Organization and Programming




Lecture 1: Representing Numbers

Analog

Water Flow (l/min)

 

Voltage (V)

 


Digital: 0 / 1

No Water / Water Flowing

Low / High Voltage


Then and Now

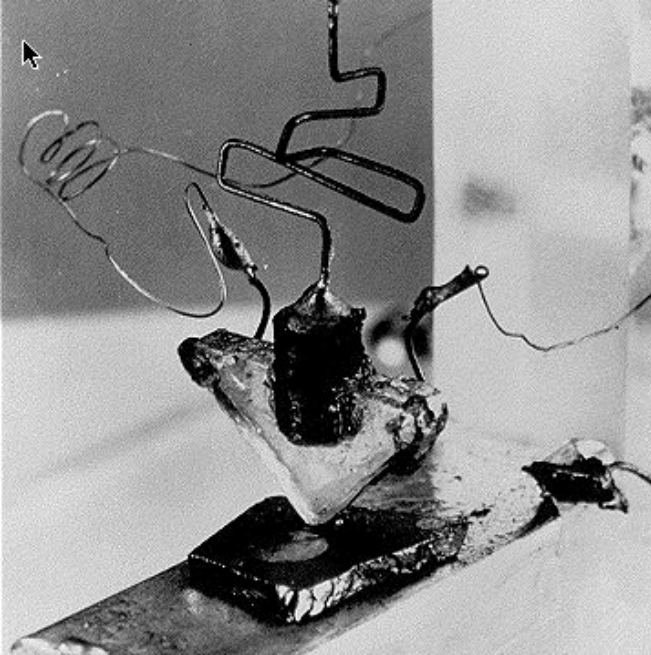

The first transistor

- One workbench at AT&T Bell Labs
- 1947
- Bardeen, Brattain, and Shockley

Then and Now

 

https://en.wikipedia.org/wiki/Apple_M4

https://en.wikipedia.org/wiki/Transistor_count


The first transistor

- One workbench at AT&T Bell Labs
- 1947
- Bardeen, Brattain, and Shockley

Apple M4


- 28 billion transistors, 3nm
- 177 square millimeters
- 4x-10x performance, 4x-6x efficiency, 8x-40x GPU, 16x Neural processing cores

Transistors 101

 


P-Transistor Off

Transistors 101

 


P-Transistor Off

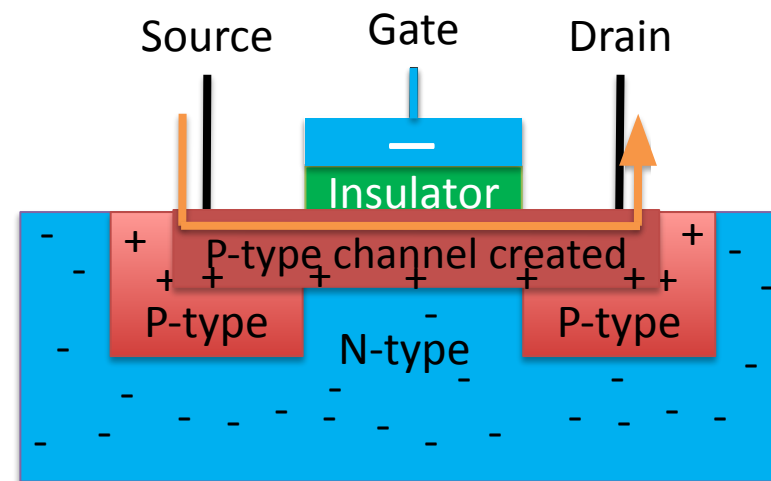


P-Transistor On

P-Transistor: **negative** charge (0!) creates conductive channel

Transistors 101

 

P-Transistor Off

 

P-Transistor On

P-Transistor: **negative** charge (0!) creates conductive channel


N-Transistor: **positive** charge (1!) creates conductive channel

2-Transistor Combination

- CMOS: combine P- and N-Transistors

Truth Table

Input	Output


 


2-Transistor Combination

- CMOS: combine P- and N-Transistors

Truth Table

Input	Output
0	1


 
 


2-Transistor Combination

- CMOS: combine P- and N-Transistors

Truth Table

Input	Output
0	1
1	0

 
 
 


2-Transistor Combination

- CMOS: combine P- and N-Transistors
- $f(a) = \dots?$

Truth Table

Input	Output
0	1
1	0

 
 
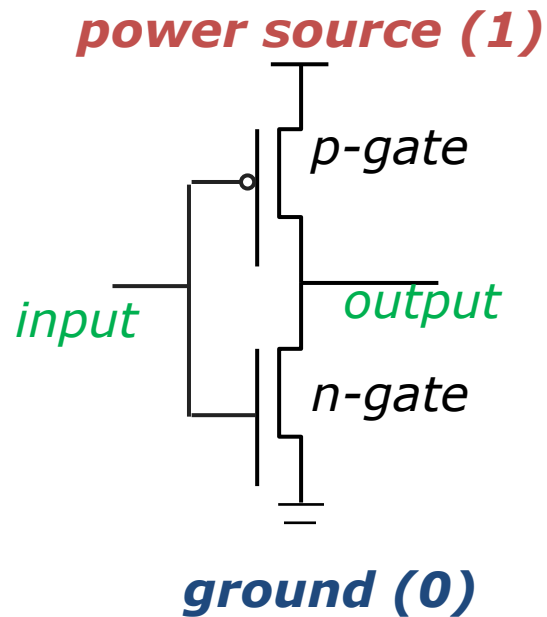


2-Transistor Combination

- CMOS: combine P- and N-Transistors
- $f(a) = \bar{a}$


Truth Table

Input	Output
0	1
1	0

 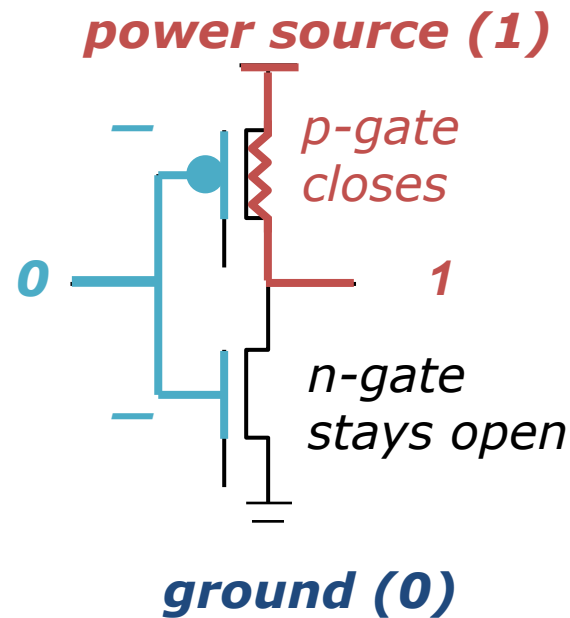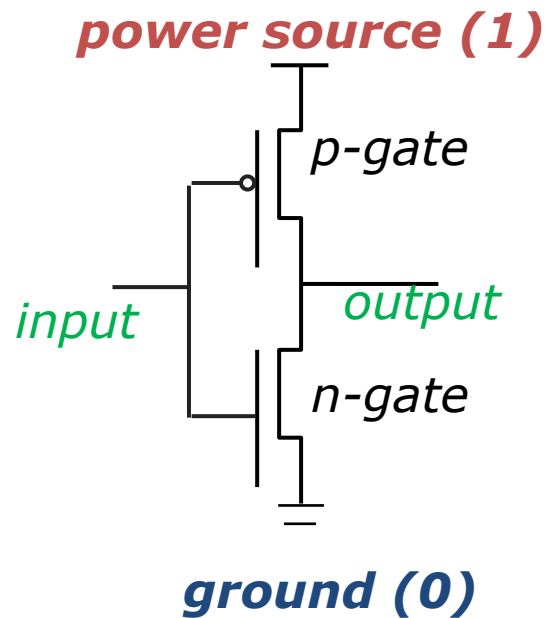




2-Transistor Combination

 - CMOS: combine P- and N-Transistors
- $f(a) = \bar{a}$
- Inverter



Truth Table


Input	Output
0	1
1	0

 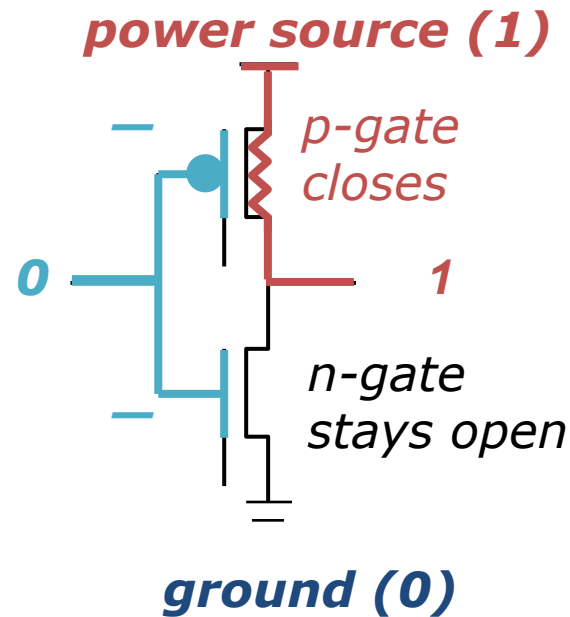 


4-Transistor Combination

Truth Table


A	B	Output
0	0	
0	1	
1	0	
1	1	

 

4-Transistor Combination

 


Truth Table

 


A	B	Output
0	0	1
0	1	
1	0	
1	1	

4-Transistor Combination


Truth Table

 

A	B	Output
0	0	1
0	1	
1	0	
1	1	

 


4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	0
1	0	
1	1	

 


4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	

 


4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

 


4-Transistor Combination

- What function is implemented?

 


Truth Table

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

 


4-Transistor Combination

- What function is implemented?

 


Truth Table

A	B	Out	$\neg$ Out
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

 


4-Transistor Combination

- $f(a, b) = \overline{a \vee b}$

 


Truth Table

A	B	Out	$\neg$ Out
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

 



4-Transistor Combination

 - $f(a, b) = \overline{a \vee b}$
- not or $\rightarrow$ NOR Gate




Truth Table


A	B	Out	$\neg$ Out
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

  

4-Transistor Combination

 


Truth Table

 


A	B	Output
0	0	1
0	1	
1	0	
1	1	

4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	1
1	0	
1	1	

 


4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	

 


4-Transistor Combination

 


Truth Table

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

 


4-Transistor Combination

- What function is implemented?

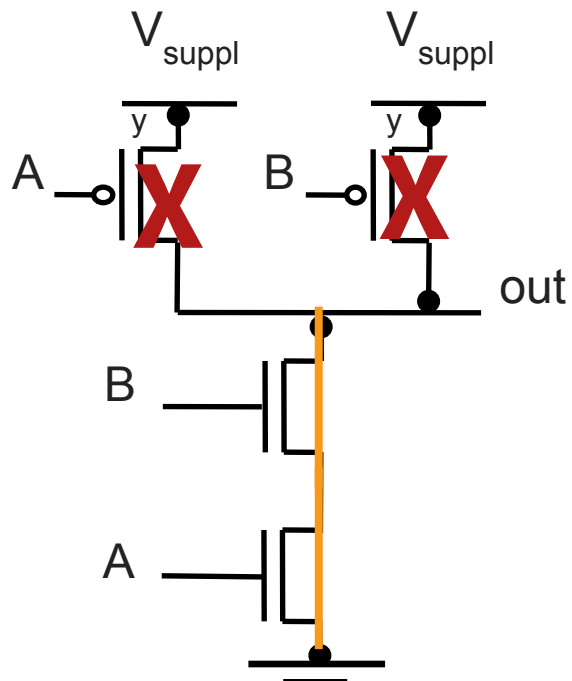


Truth Table

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

 

4-Transistor Combination

- What function is implemented?

 


Truth Table

A	B	Out	$\neg$ Out
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

4-Transistor Combination

- $f(a, b) = \overline{a \wedge b}$

 


Truth Table

A	B	Out	$\neg$ Out
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1


4-Transistor Combination

 - $f(a, b) = \overline{a \wedge b}$
- not and $\rightarrow$ NAND gate




Truth Table


A	B	Out	$\neg$ Out
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

 


1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$


1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

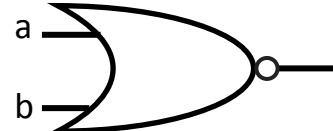NOR: a  b $f(a, b) = \overline{a \vee b}$


1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 
NOR: a  b $f(a, b) = \overline{a \vee b}$

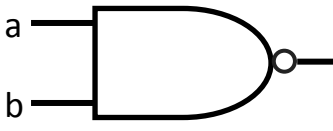
NAND: a  b $f(a, b) = \overline{a \wedge b}$

1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 
NOR: a  b $f(a, b) = \overline{a \vee b}$

 
NAND: a  b $f(a, b) = \overline{a \wedge b}$

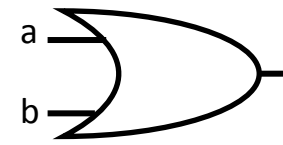
OR: a  b $f(a, b) = a \vee b$
 $= a + b$

1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 
NOR: a  b $f(a, b) = \overline{a \vee b}$

 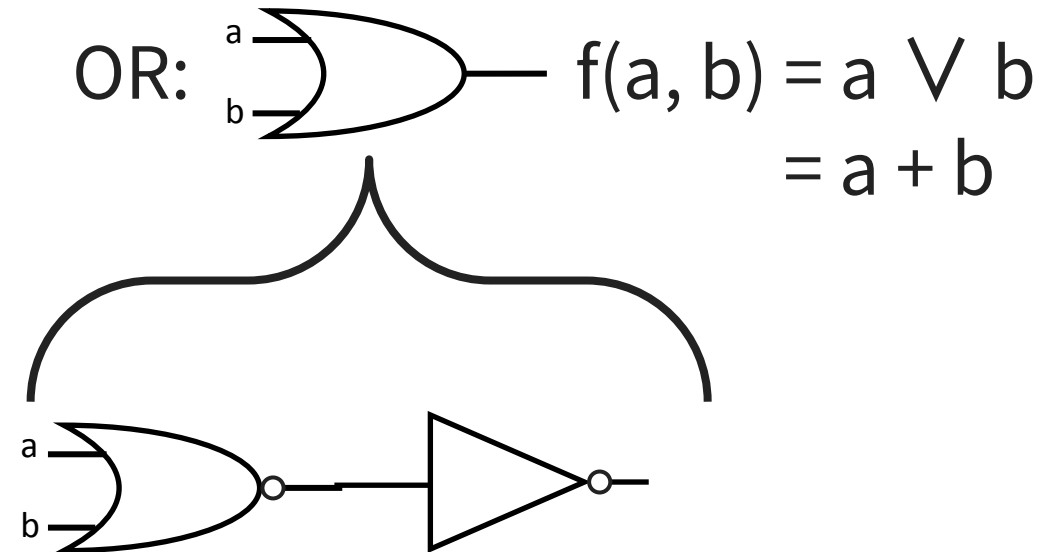
NAND: a  b $f(a, b) = \overline{a \wedge b}$





1 and 2 Input Logic Gates

 Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 
NOR: a  b $f(a, b) = \overline{a \vee b}$

 
NAND: a  b $f(a, b) = \overline{a \wedge b}$

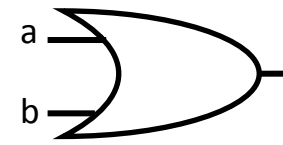
OR: a  b $f(a, b) = a \vee b$
 $= a + b$

 
AND: a  b $f(a, b) = a \wedge b$
 $= a \times b$
 $= ab$


1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 NOR: a  b $f(a, b) = \overline{a \vee b}$

 
NAND: a  b $f(a, b) = \overline{a \wedge b}$

 
OR: a  b $f(a, b) = a \vee b$
 $= a + b$

 
AND: a  b $f(a, b) = a \wedge b$

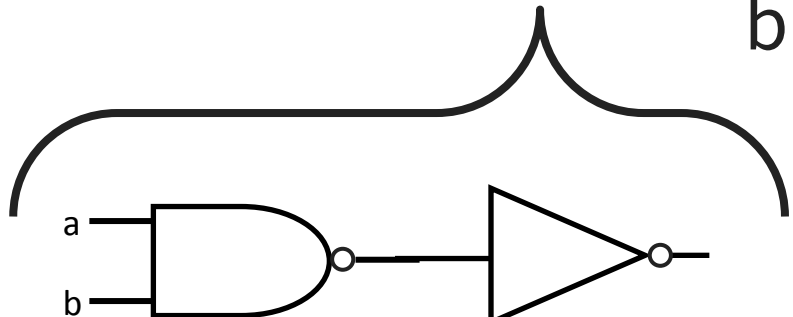
 $= a \times b$
 $= ab$


1 and 2 Input Logic Gates

 
Inverter: a  $f(a) = \bar{a}$
 $= \neg a$

 NOR: a  $f(a, b) = \overline{a \vee b}$

 NAND: a  $f(a, b) = \overline{a \wedge b}$

 XOR: a  $f(a, b) = a \oplus b$
 $= \bar{a}b \vee a\bar{b}$

 OR: a  $f(a, b) = a \vee b$
 $= a + b$

 AND: a  $f(a, b) = a \wedge b$
 $= a \times b$
 $= ab$

Identities

$$a \vee 0 =$$

$$a \vee 1 =$$

$$a \vee \bar{a} =$$

$$a \wedge 0 =$$

$$a \wedge 1 =$$

$$a \wedge \bar{a} =$$

Truth Table

a	$a \vee 0$
0	0
1	1



Identities

$$a \vee 0 = a$$

$$a \vee 1 =$$

$$a \vee \bar{a} =$$

$$a \wedge 0 =$$

$$a \wedge 1 =$$

$$a \wedge \bar{a} =$$

Truth Table

a	$a \vee 0$
0	0
1	1

Identities

$$a \vee 0 = a$$

$$a \vee 1 = 1$$

$$a \vee \bar{a} =$$

$$a \wedge 0 =$$

$$a \wedge 1 =$$

$$a \wedge \bar{a} =$$



Identities

$$a \vee 0 = a$$

$$a \vee 1 = 1$$

$$a \vee \bar{a} = 1$$

$$a \wedge 0 =$$

$$a \wedge 1 =$$

$$a \wedge \bar{a} =$$



Identities

$$a \vee 0 = a$$

$$a \vee 1 = 1$$

$$a \vee \bar{a} = 1$$

$$a \wedge 0 = 0$$

$$a \wedge 1 =$$

$$a \wedge \bar{a} =$$

Truth Table

a	$a \wedge 1$
0	0
1	1



Identities

$$a \vee 0 = a$$

$$a \vee 1 = 1$$

$$a \vee \bar{a} = 1$$

$$a \wedge 0 = 0$$

$$a \wedge 1 = a$$

$$a \wedge \bar{a} =$$

Truth Table

a	$a \wedge 1$
0	0
1	1



Identities

$$a \vee 0 = a$$

$$a \vee 1 = 1$$

$$a \vee \bar{a} = 1$$

$$a \wedge 0 = 0$$

$$a \wedge 1 = a$$

$$a \wedge \bar{a} = 0$$



DeMorgan's Law

$$\overline{a \wedge b} = \overline{a} \vee \overline{b}$$

$$\overline{a \vee b} = \overline{a} \wedge \overline{b}$$



Distributive Property

$$a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$$



Distributive Property

$$a \wedge (b \vee c) = (a \wedge b) \vee (a \wedge c)$$


$$a (b + c) = ab + ac$$



Which Gate is this?



PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	
0	1	
1	0	
1	1	

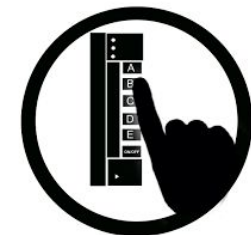 


PollEv.com/cs3410


Which Gate is this?

PollEV Question #1


 
- (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

 

A	B	Out
0	0	0
0	1	
1	0	
1	1	

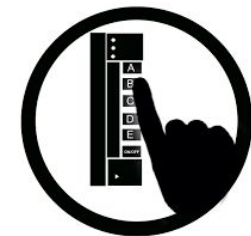 


PollEv.com/cs3410

Which Gate is this?




PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	0
0	1	1
1	0	
1	1	

   


PollEv.com/cs3410

Which Gate is this?




PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	

   


PollEv.com/cs3410

Which Gate is this?



PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

  


[PollEv.com/cs3410](https://pollev.com/cs3410)

Which Gate is this?


PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

 


[PollEv.com/cs3410](https://pollev.com/cs3410)

Which Gate is this?

PollEV Question #1


 
- (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

$\bar{a}b \vee$

  


[PollEv.com/cs3410](https://pollev.com/cs3410)

Which Gate is this?

PollEV Question #1


 
- (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Truth Table

$\bar{a}b \vee a\bar{b}$

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

  


[PollEv.com/cs3410](https://poll-ev.com/cs3410)

Which Gate is this?

PollEV Question #1

 - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 




$$\bar{a}b \vee a\bar{b}$$

minterms!

Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

 

PollEv.com/cs3410

Truth Table to Boolean Formula with SOP

- **Sum-Of-Product (SOP) or Disjunctive Normal Form (DNF)**

Disjunction

$$\underline{\bar{a}b} \downarrow \vee \underline{\bar{a}b}$$

Truth Table to Boolean Formula with SOP

- **Sum-Of-Product (SOP) or Disjunctive Normal Form (DNF)**

Disjunction

$$\begin{array}{c} \downarrow \\ \underline{\bar{a}b} \vee \underline{a\bar{b}} \\ \bar{a}b + a\bar{b} \\ \begin{array}{ccc} \uparrow & \uparrow & \uparrow \\ & \text{Sum} & \\ \text{Products} & & \end{array} \end{array}$$

Truth Table to Boolean Formula with SOP

Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

- **Sum-Of-Product (SOP)** or **Disjunctive Normal Form (DNF)**
- **minterms:**
product of (inverted) inputs

Disjunction

$$\begin{array}{c} \downarrow \\ \bar{a}b \vee a\bar{b} \\ \bar{a}b + a\bar{b} \\ \begin{array}{ccc} \uparrow & \uparrow & \uparrow \\ \text{Products} & \text{Sum} & \end{array} \end{array}$$

Truth Table to Boolean Formula with POS

Truth Table

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

- **Sum-Of-Product (SOP)** or **Disjunctive Normal Form (DNF)**
- **minterms:**
product of (inverted) inputs
- **Product-Of-Sum (POS)** or **Conjunctive Normal Form (CNF)**
- **maxterms:**
sum of (inverted) inputs

Disjunction

$$\begin{array}{c} \downarrow \\ \bar{a}b \vee a\bar{b} \\ \bar{a}b + a\bar{b} \\ \uparrow \quad \uparrow \quad \uparrow \\ \text{Products} \quad \text{Sum} \end{array}$$

$$\underline{(a + b)} \underline{(\bar{a} + \bar{b})}$$

Truth Table to Boolean Formula with POS

Truth Table

A	B	Out	$\neg$ Out
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

$$\overline{f(a, b)} = \bar{a}\bar{b} + ab$$

- **Sum-Of-Product (SOP)** or **Disjunctive Normal Form (DNF)**
- **minterms:**
find rows where output is 1
- **Product-Of-Sum (POS)** or **Conjunctive Normal Form (CNF)**
- **maxterms:**
sum of (inverted) inputs

Disjunction

$$\begin{array}{c} \downarrow \\ \bar{a}b \vee a\bar{b} \\ \bar{a}b + a\bar{b} \\ \uparrow \quad \uparrow \quad \uparrow \\ \text{Products} \quad \text{Sum} \end{array}$$

$$\underline{(a + b)} \underline{(\bar{a} + \bar{b})}$$

Truth Table to Boolean Formula with POS

Truth Table

A	B	Out	$\neg$ Out
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

- **Sum-Of-Product (SOP)** or **Disjunctive Normal Form (DNF)**
- **minterms:**
find rows where output is 1
- **Product-Of-Sum (POS)** or **Conjunctive Normal Form (CNF)**
- **maxterms:**
sum of (inverted) inputs

Disjunction

$$\begin{array}{c} \downarrow \\ \underline{\bar{a}b} \vee \underline{a\bar{b}} \\ \bar{a}b + a\bar{b} \\ \uparrow \quad \uparrow \quad \uparrow \\ \text{Products} \quad \text{Sum} \end{array}$$

$$\overline{f(a, b)} = \bar{a}\bar{b} + ab$$

$$f(a, b) = \overline{\bar{a}\bar{b} + ab} = \underline{(a + b)} \underline{(\bar{a} + \bar{b})}$$

Sum-Of-Product Practice



Sum-Of-Product Practice

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

- 1) Write **minterms**
- 2) **sum of products:**
 - OR of all minterms where out=1

Logic Implementation

- How to implement a desired logic function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1) Write **minterms**

2) **sum of products:**

- OR of all minterms where out=1

- E.g. $out = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c$

Logic Implementation

- How to implement a desired logic function?


a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1) Write **minterms**

 2) **sum of products:**

- OR of all minterms where out=1


- E.g. $out = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c$



corollary: **any** combinational circuit *can be* implemented in two levels of logic
(ignoring inverters)


Multiplexor

 - Select one of two inputs
- Ternary operator in C: `sel? b : a`



Multiplexor

 - Select one of two inputs
- Ternary operator in C: `sel ? b : a`




Truth Table

sel	b	a	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Multiplexor

 - Select one of two inputs
- Ternary operator in C: `sel ? b : a`




$$\overline{s}ba + \overline{s}ba + sb\overline{a} + sba$$

Truth Table

s	b	a	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Multiplexor

 - Select one of two inputs
- Ternary operator in C: `sel ? b : a`




$$\overline{s}ba + \overline{s}b\overline{a} + sb\overline{a} + sba = \overline{s}a + sb$$

Truth Table


s	b	a	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Multiplexor

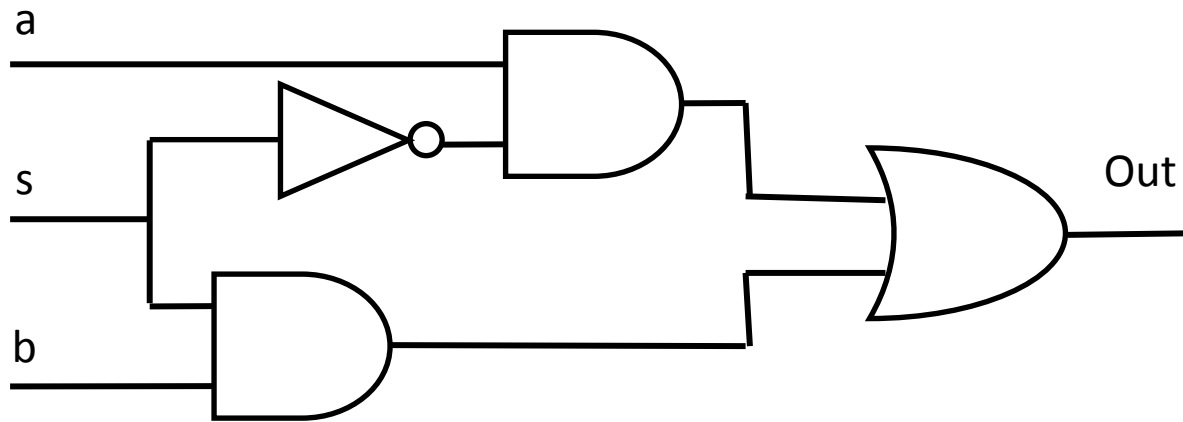- Select one of two inputs
- Ternary operator in C: `sel? b : a`


 
$$\bar{s}ba + \bar{s}ba + sb\bar{a} + sba = \bar{s}a + sb$$



Truth Table


s	b	a	Out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Binary Addition



Adding Binary Numbers
 
$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \hline \end{array}$$




Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \hline \end{array}$$


$+1$

$$1_{10}$$

 

Adding Binary Numbers

 
$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$
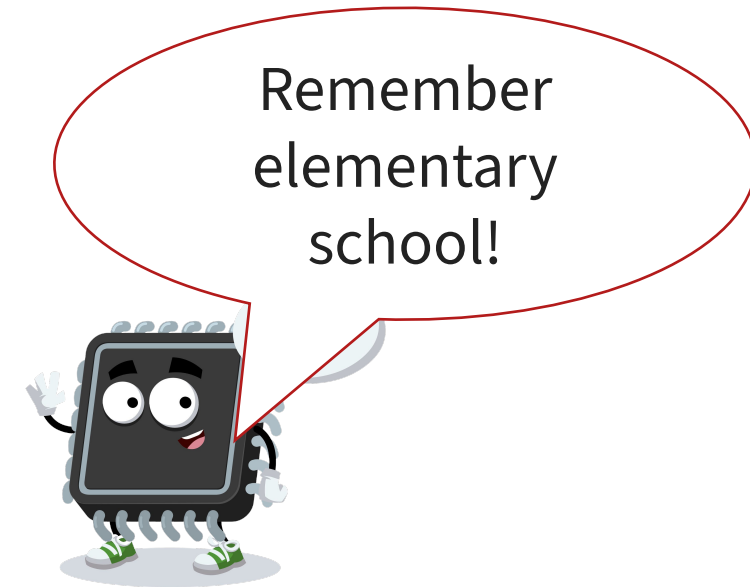
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \hline \end{array}$$




Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \hline 41_{10} \end{array}$$

(Note: A red circle highlights the '+1' in the original image, indicating a carry or addition step.)

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \hline 1_2 \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \hline 01_2 \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \hline 001_2 \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \hline 1001_2 \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \textcircled{+1} \\ \hline 01001_2 \end{array}$$



Adding Binary Numbers

$$\begin{array}{r} 24_{10} \\ + 17_{10} \\ \textcircled{+1} \\ \hline 41_{10} \end{array}$$

 
$$\begin{array}{r} 11000_2 \\ + 10001_2 \\ \textcircled{+1} \\ \hline 101001_2 \end{array}$$



Binary Addition

- Binary addition requires
 - Add of *two bits* PLUS *carry-in*
 - Also, *carry-out* if necessary

1-bit Half Adder

 

A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- No carry-in


PollEv.com/cs3410




PollEV Question

What is the equation for C_{out} ?

 - a) $A + B$
- b) AB
- c) $A \oplus B$
- d) $A + !B$
- e) $!A!B$



1-bit Half Adder

 

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- No carry-in

A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

PolLEV Question #3

What is the equation for C_{out} ?

a) $A + B$


b) AB

c) $A \oplus B$

d) $A + !B$

e) $!A!B$

1-bit Half Adder

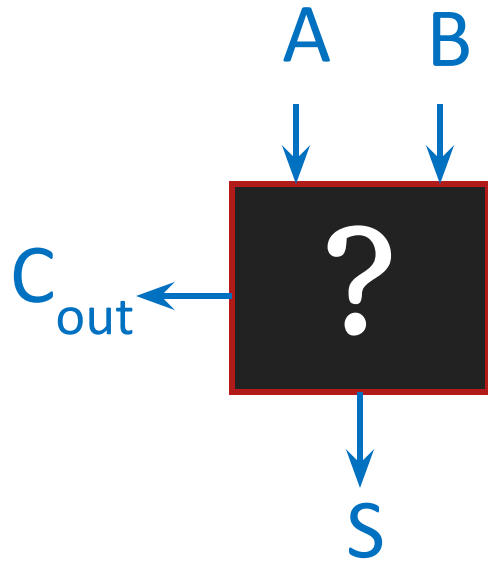

A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- No carry-in

0	0	0	1
0	0	1	1
<u>+ 0</u>	<u>+ 1</u>	<u>+ 0</u>	<u>+ 1</u>
0	1	1	0

S = one input equals 1

C_{out} = two inputs equal 1

1-bit Half Adder


 


- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- No carry-in


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_{out} = AB$$

  

1-bit Full Adder

 


A	B	C _{in}	C _{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- Can be cascaded

- Fill in Truth Table
- Create Sum-of-Product Form
- Draw the Circuits

1-bit Full Adder

 

A	B	C _{in}	C _{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- Can be cascaded


Pollev.com/cs3410




Pollev Question #4

What is the equation for C_{out} ?

 - a) $A + B + C_{in}$
- b) $\neg A + \neg B + \neg C_{in}$
- c) $A \oplus B \oplus C_{in}$
- d) $\overline{A}BC + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$
- e) $\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$



1-bit Full Adder

 

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- Can be cascaded


A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

PolLEV Question #4

What is the equation for C_{out}?

- a) $A + B + C_{in}$
- b) $\neg A + \neg B + \neg C_{in}$
- c) $A \oplus B \oplus C_{in}$
- d) $\overline{A}BC + \overline{A}\overline{B}C + A\overline{B}\overline{C} + ABC$
- e) $\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$

1-bit Full Adder

 


- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry-out
- Can be cascaded


A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$
 
$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$





4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- 3 + 2 = 5
- Carry-out ☐ result > 4 bits

4-bit Adder

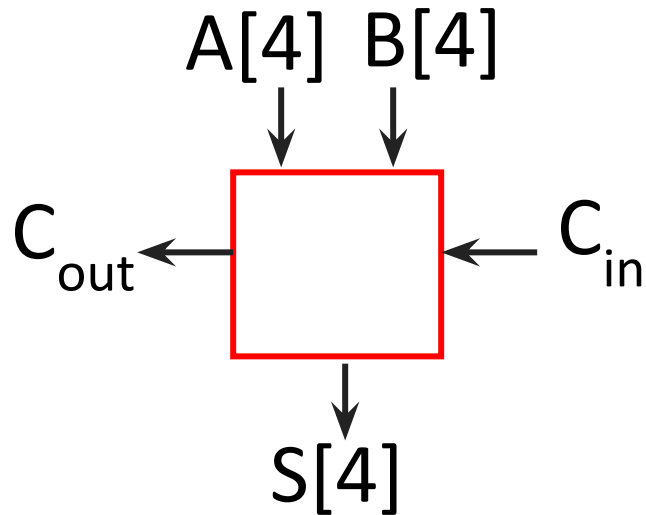
 


**Build it
and
box it!**
(Theme of 3410)

PollEV Question #5

What's the largest **sum** you can calculate with a 4 bit adder?
(Give your answer in base 10. Assume unsigned numbers)

  - a) 4
- b) 1,111
- c) 15
- d) 16
- e) 4000




Pollev.com/cs3410



PolIEV Question #5

What's the largest **sum** you can calculate with a 4 bit adder?
(Give your answer in base 10. Assume unsigned numbers)

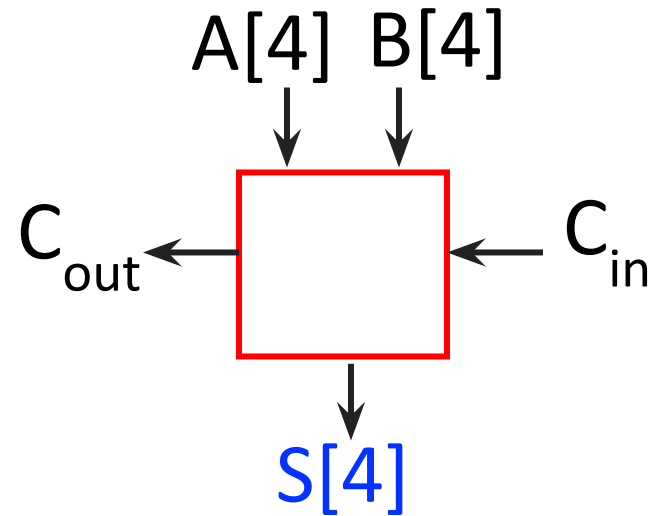- a) 4
- b) 1,111
- c) 15
- d) 16
- e) 4000



Binary Subtraction

Why create a new circuit?

Just use addition using two's complement math


How?

Binary Subtraction

Two's Complement Subtraction

- Subtraction is addition with a negated operand
 - Negation is done by **inverting all bits** and **adding one**
 
$$A - B = A + (-B) = A + (\overline{B} + 1)$$




Binary Subtraction

Two's Complement Subtraction

- Subtraction is addition with a negated operand
 - Negation is done by **inverting all bits** and **adding one**
 
$$A - B = A + (-B) = A + (\bar{B} + 1) \quad \text{E.g. } 7 - 3 = 4 \rightarrow 7 + (-3) = 4$$




Binary Subtraction

Two's Complement Subtraction

- Subtraction is addition with a negated operand
 - Negation is done by **inverting all bits** and **adding one**

$$A - B = A + (-B) = A + (\bar{B} + 1)$$

 

Add or subtract with
XOR gate

sub?	B_0	new B_0
0	0	0
0	1	1
1	0	1
1	1	0

if subtracting, invert B_0

Binary Subtraction

Two's Complement Subtraction


- Subtraction is addition with a negated operand
 - Negation is done by **inverting all bits** and **adding one**

$$A - B = A + (-B) = A + (\bar{B} + 1)$$

Add or subtract with
XOR gate

sub?	B_0	new B_0
0	0	0
0	1	1
1	0	1
1	1	0

if subtracting, invert B_0

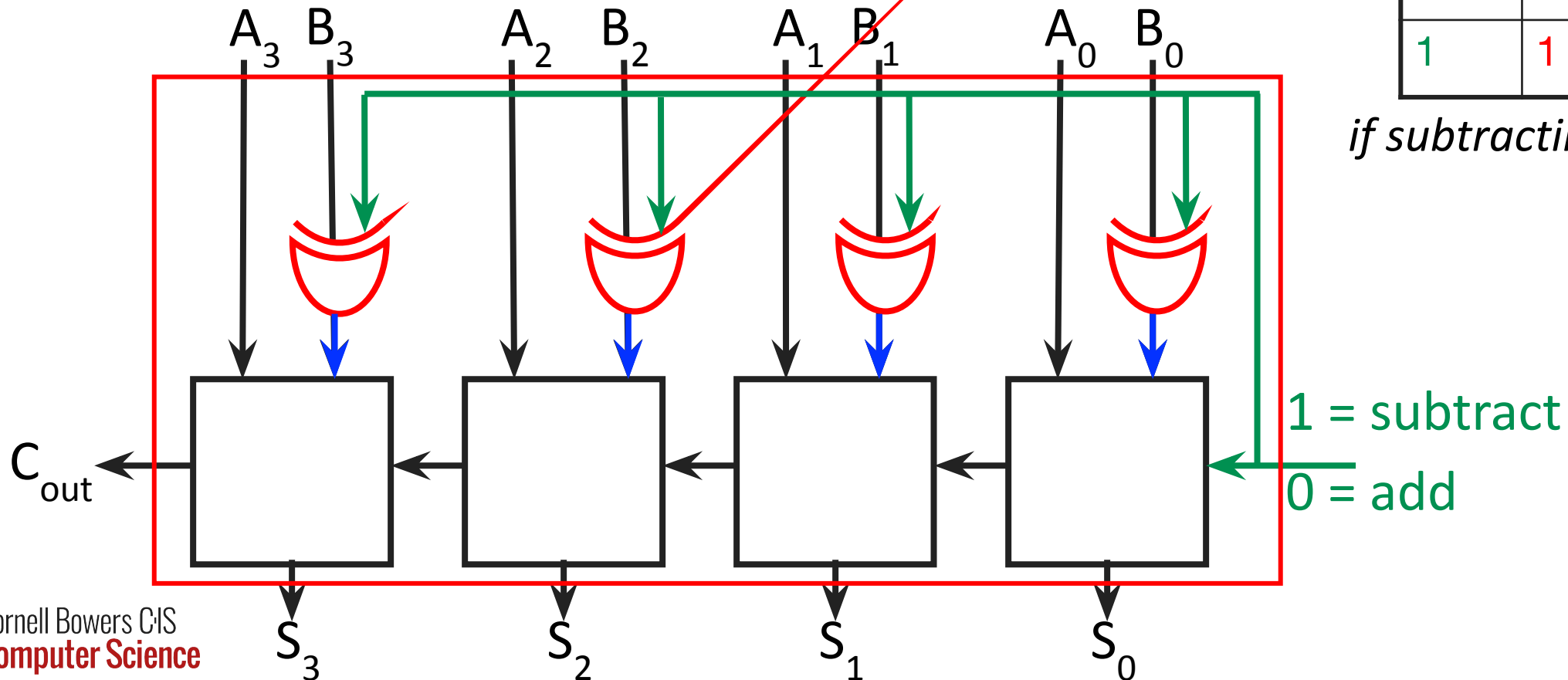

Binary Subtraction


Two's Complement Subtraction

- Subtraction is addition with a negated operand
 - E.g. $6 - 7 = -1$ $\square$ $6 + (-7) = -1$

Add or subtract with
XOR gate

sub?	B_0	new B_0
0	0	0
0	1	1
1	0	1
1	1	0

if subtracting, invert B_0

 

Binary Subtraction


Two's Complement Subtraction

- Subtraction is addition with a negated operand
 - Addition still works! E.g. 2 + 5 = 7


Add or subtract with
XOR gate

sub?	B_0	new B_0
0	0	0
0	1	1
1	0	1
1	1	0


if subtracting, invert B_0

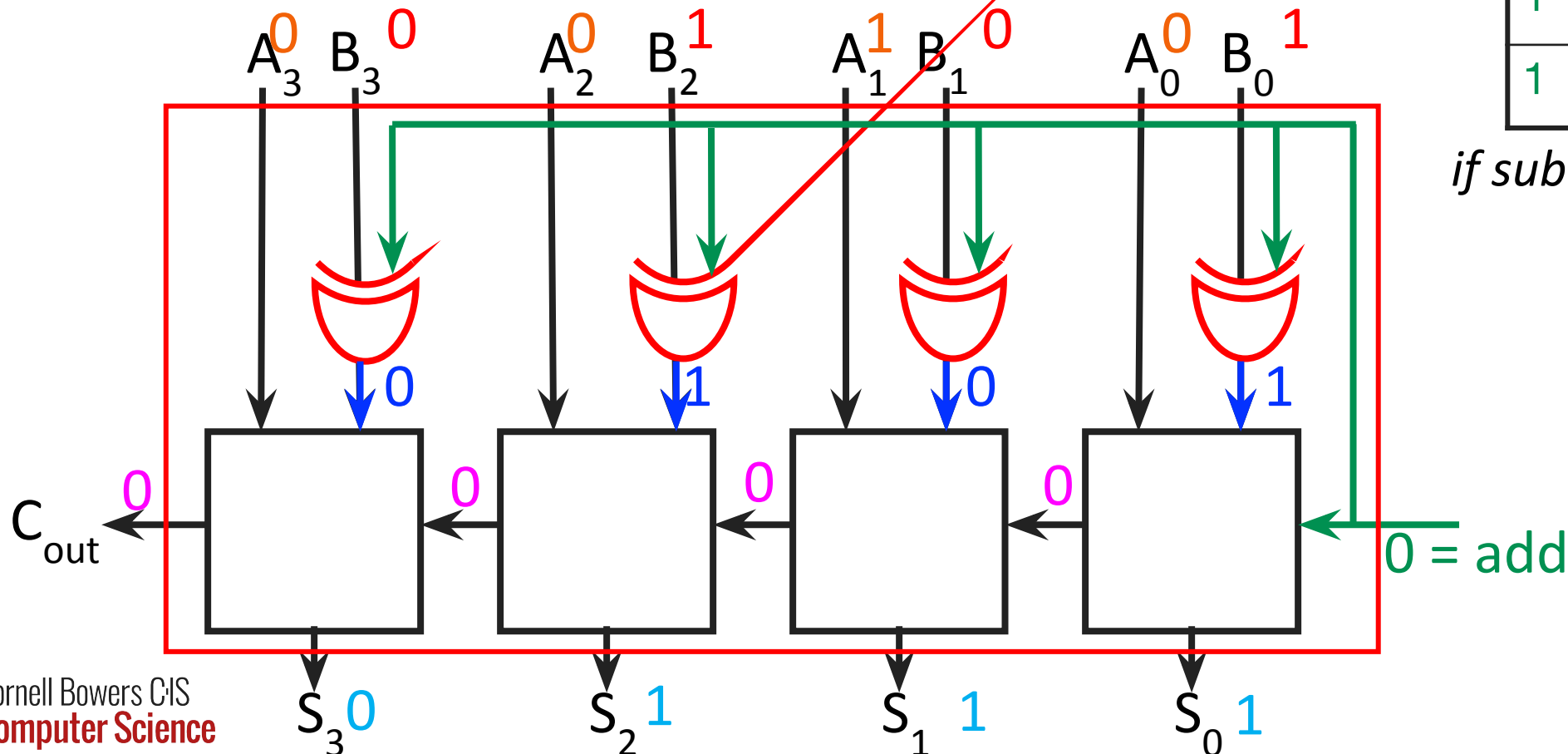


4-bit Adder with Two's Complement

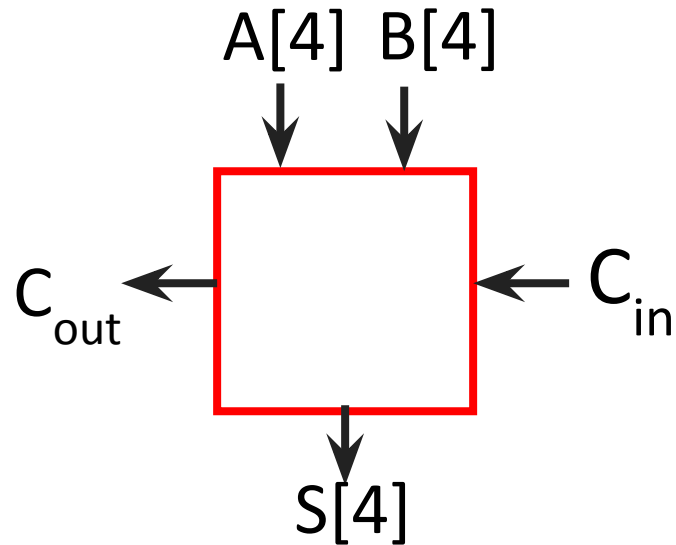


8-bit Adder with Two's Complement

 


8-bit Adder with Two's Complement

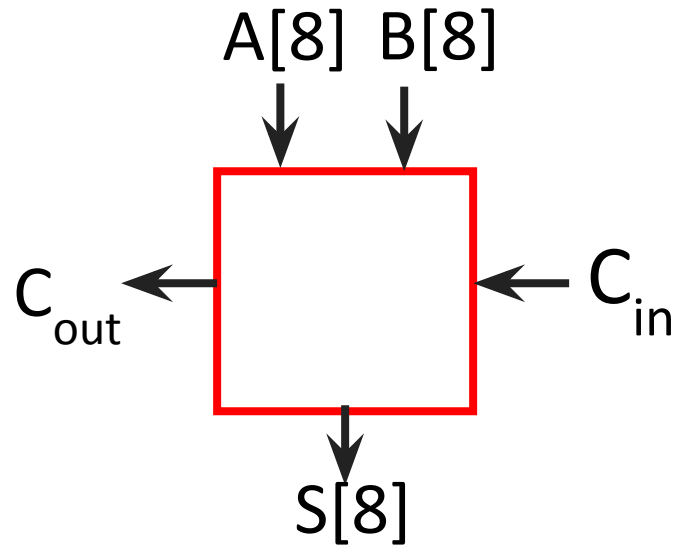


32-bit Adder with Two's Complement

 

32-bit Adder with Two's Complement

 

64-bit Adder with Two's Complement

 

64-bit Adder with Two's Complement

