

CS 3410 Lab 4

Spring 2026



Agenda

1 Circuit Waveform Practice


2 CPU Overview

3 Decoding and Encoding

4 Assignment Tips

Circuit Waveform Practice

D Flip-Flop

 


- Edge Triggered (positive or negative). The one above is negative-edge triggered.
- First D-Latch allows input to go through ($D \rightarrow X$) when clock is high.
- Second D-Latch allows input to go through ($X \rightarrow Q$) when clock is low.
- Combining these two means that ($D \rightarrow Q$) occurs when clock falls ($1 \rightarrow 0$).

D Flip-Flop Continued

Clock = 1:

L1 transparent, L2 opaque

 
When CLK rises ($0 \rightarrow 1$), now X can change,
Q does not change anymore, X gets value D.



Clock = 0:



L1 opaque, L2 transparent

 When CLK falls ($1 \rightarrow 0$), now Q can change,
X cannot change anymore, Q gets value X.



D Flip-Flop Example

  
- X copies D value when clk is high.
- Q copies X value when clk is low.
- The changes are slightly delayed below.



Remember to mirror logic when doing a positive-edge triggered D Flip Flop.


CPU Overview

A 5-Stage RISC Processor

 

Stage 1: Fetch

F: Fetch

 

Fetches instruction found at the PC.


Instruction Memory:

- Stores instructions to execute on the CPU.

Program Counter (PC):

- Points to the next instruction to execute.
- Increments by 4 (1 word) to get next instruction.
- Or by an immediate when we need to jump or branch.

Stage 2: Decode

 

Decode parts of the instruction to decide how to execute it.

Register File:

- Extract values for `rs1`, `rs2` and `rd` registers.
- Extract immediate, sign-extend to convert to 64-bit number.


Note: Not all instructions will use `rs1`, `rs2` or `rd` registers.



- Calculate PC + offset. This may or may not be used depending on the instruction.


- Performs an operation using `rs1` and either `rs2` or `immediate`.
- Type of op also depends on instruction.

Stage 4: Memory

 

Data Memory:

 - May carry out either a **read** or **write** operation, depending on instruction.
- If **write**, this stage writes data from a register to a particular address.
- If **read**, it reads from a particular location and forwards it to the next stage.



- For **load** instructions, write the output from memory to the 'Write data' register.
- For arithmetic instructions (like **add**), write back the ALU output to the 'Write data' register.

Note: Not all instructions will use this stage (think store instructions).

Decoding and Encoding

I-type Instructions

31 – 20	19 – 15	14 – 12	11 – 7	6 – 0
imm[11:0]	rs1	funct3	rd	opcode

- ``addi`` and ``andi`` are examples of I-type instructions

I-type Instructions

31 – 20	19 – 15	14 – 12	11 – 7	6 – 0
imm[11:0]	rs1	funct3	rd	opcode

- ``addi`` and ``andi`` are examples of I-type instructions
- We use the **opcode** and **funct3** (and sometimes funct7) bits of the instruction to decide how the instruction will execute

I-type Instructions

31 – 20	19 – 15	14 – 12	11 – 7	6 – 0
imm[11:0]	rs1	funct3	rd	opcode

- ``addi`` and ``andi`` are examples of I-type instructions
- We use the **opcode** and **funct3** (and sometimes funct7) bits of the instruction to decide how the instruction will execute

Instruction	opcode	funct3
<code>addi</code>	0010011	000
<code>andi</code>	0010011	111

Relevant opcode and funct3 bits for `addi` and `andi`

Assignment Tips

Some useful tips for the assignment

- Use the **`info` struct** to store relevant instruction data between processor stages, including what type of instruction it is. We provide a mapping from instructions to integers via the `#define` macros in `logic.h`.
- Think how the **`memory` stage** will be used by different instructions (**hint: some won't need to read or write!**). Sometimes this Memory stage will be a no-op that propagates information to the Writeback stage from the ALU.
- Consider how your writeback stage should update the state of the program (the PC counter) to prepare it for the next instruction. (maybe **PC + 4**? maybe **PC + offset**?)



How to test your implementation

- Make sure you clone the assignment repo and your terminal is under that folder
- To test your implementation for the assignment, follow the following steps:
 - Compile your implementation with ***“rv make”***.
 - Write a test script in RISC-V assembly, let's call it ***“prog.s”***.
 - Compile the test script using ***“rv asbin prog.s”***.
 - Run the implementation using ***“rv qemu runner < prog.bin”***.
 - You can also initialize the registers: ***“rv qemu runner 1@0x1 < prog.bin”***.
- When doing multiple tests, highly recommend using the **test_parser.py** script, through ***“rv python3 test_parser.py tests.txt”***
- All this information (and more) can be found in the assignment instruction.

