

Processor

Prof. Hakim Weatherspoon

CS 3410, Spring 2015

Computer Science

Cornell University

See P&H Chapter: 4.1-4.4, 1.6, Appendix B

Announcements

Project Partner finding assignment on CMS

No official office hours over break

Lab1 due tomorrow

HW1 Help Sessions Wed, Feb 18 and Sun, Feb 21

Announcements

Make sure to go to **your** Lab Section this week

Lab2 due in class this week (it is **not** homework)

Lab1: Completed Lab1 due **tomorrow** Friday, Feb 13th, **before** winter break

Note, a **Design Document** is due when you submit Lab1 final circuit

Work **alone**

Save your work!

- **Save often.** Verify file is non-zero. Periodically save to Dropbox, email.
- Beware of MacOSX 10.5 (leopard) and 10.6 (snow-leopard)

Homework1 is out

Due a week before prelim1, Monday, February 23rd

Work on problems incrementally, as we cover them in lecture (i.e. part 1)

Office Hours for help

Work **alone**

Work alone, **BUT** use your resources

- Lab Section, Piazza.com, Office Hours
- Class notes, book, Sections, CSUGLab

Announcements

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2015sp/schedule.html>
- Slides and Reading for lectures
- Office Hours
- ***Pictures of all TAs***
- Homework and Programming Assignments
- **Dates to keep in Mind**
 - **Prelims: Tue Mar 3rd and Thur April 30th**
 - ***Lab 1: Due this Friday, Feb 13th before Winter break***
 - Proj2: Due Thur Mar 26th before Spring break
 - Final Project: Due when final would be (not known until Feb 14t

Schedule is subject to change

Collaboration, Late, Re-grading Policies

“Black Board” Collaboration Policy

- Can discuss approach together on a “black board”
- Leave and write up solution independently
- Do not copy solutions

Late Policy

- Each person has a total of **four** “slip days”
- Max of **two** slip days for any individual assignment
- Slip days deducted first for *any* late assignment, cannot selectively apply slip days
- For projects, slip days are deducted from all partners
- **25%** deducted per day late after slip days are exhausted

Regrade policy

- Submit written request to lead TA,
and lead TA will pick a different grader
- Submit another written request,
lead TA will regrade directly
- Submit yet another written request for professor to regrade.

Goals for today

MIPS Datapath

- Memory layout
- Control Instructions

Performance

- How fast can we make it?
- CPI (Cycles Per Instruction)
- MIPS (Instructions Per Cycle)
- Clock Frequency

MIPS Instruction Types

Arithmetic/Logical

- R-type: result and two source registers, shift amount
- I-type: 16-bit immediate with sign/zero extension

Memory Access

- load/store between registers and memory
- word, half-word and byte operations

Control flow

- conditional branches: pc-relative addresses
- jumps: fixed offsets, register absolute

Memory Instructions

101011001010000100000000000000100

I-Type

op rs rd offset


6 bits 5 bits 5 bits 16 bits

base + offset
addressing

op	mnemonic	description
0x23	LW rd, offset(rs)	$R[rd] = \text{Mem}[\text{offset} + R[rs]]$
0x2b	SW rd, offset(rs)	$\text{Mem}[\text{offset} + R[rs]] = R[rd]$

signed
offsets

Memory Operations

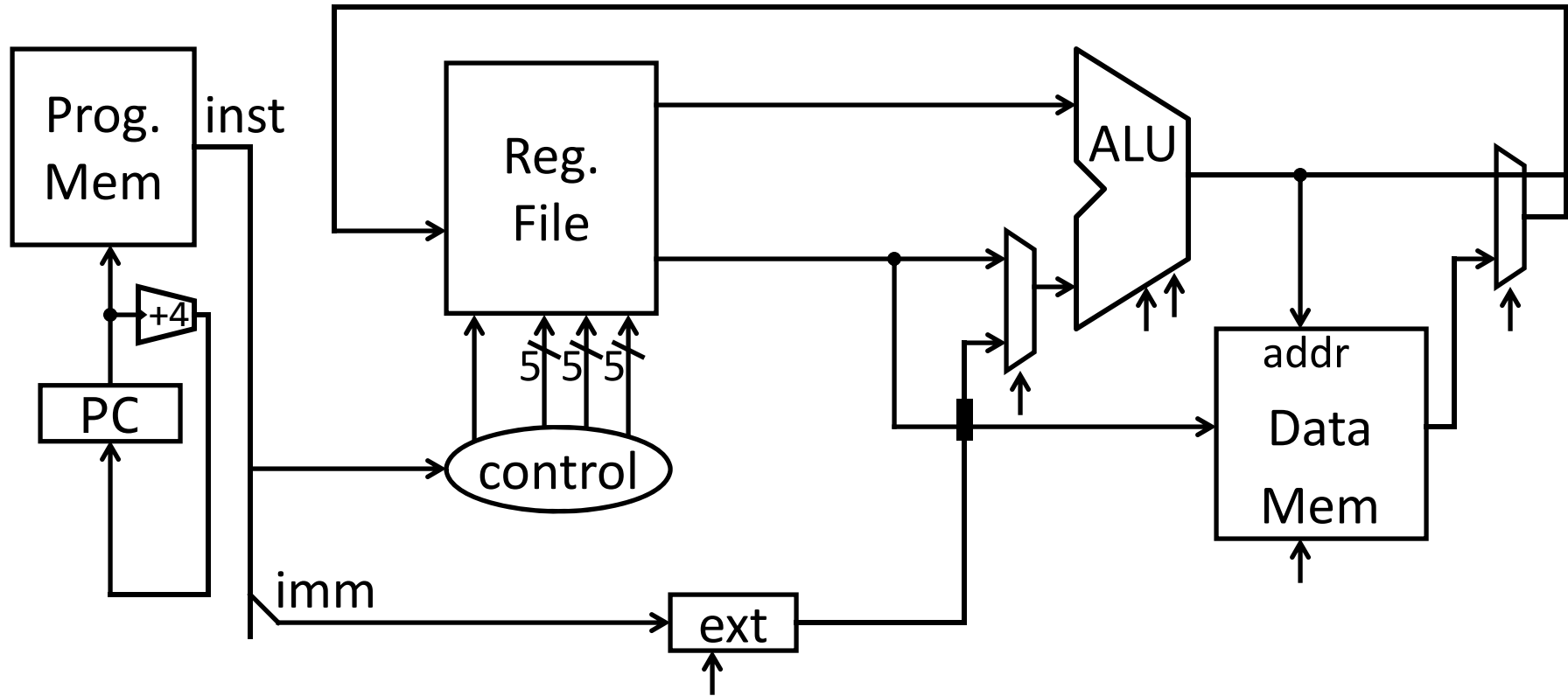

Memory Instructions

101011001010000100000000000000100

op rs rd offset


6 bits 5 bits 5 bits 16 bits

op	mnemonic	description
0x20	LB rd, offset(rs)	$R[rd] = \text{sign_ext}(\text{Mem}[\text{offset}+R[rs]])$
0x24	LBU rd, offset(rs)	$R[rd] = \text{zero_ext}(\text{Mem}[\text{offset}+R[rs]])$
0x21	LH rd, offset(rs)	$R[rd] = \text{sign_ext}(\text{Mem}[\text{offset}+R[rs]])$
0x25	LHU rd, offset(rs)	$R[rd] = \text{zero_ext}(\text{Mem}[\text{offset}+R[rs]])$
0x23	LW rd, offset(rs)	$R[rd] = \text{Mem}[\text{offset}+R[rs]]$
0x28	SB rd, offset(rs)	$\text{Mem}[\text{offset}+R[rs]] = R[rd]$
0x29	SH rd, offset(rs)	$\text{Mem}[\text{offset}+R[rs]] = R[rd]$
0x2b	SW rd, offset(rs)	$\text{Mem}[\text{offset}+R[rs]] = R[rd]$


Endianness

Endianness: Ordering of bytes within a memory word

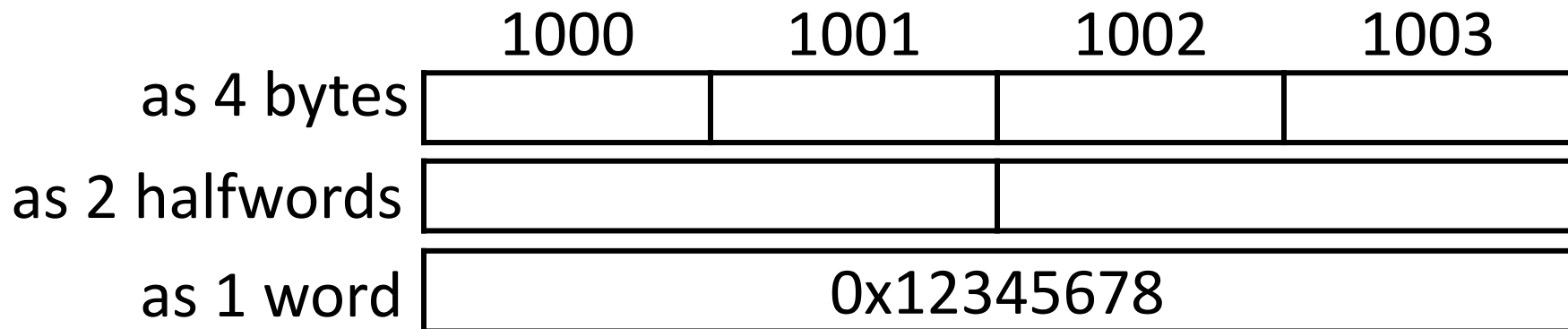Little Endian = least significant part first (MIPS, x86)



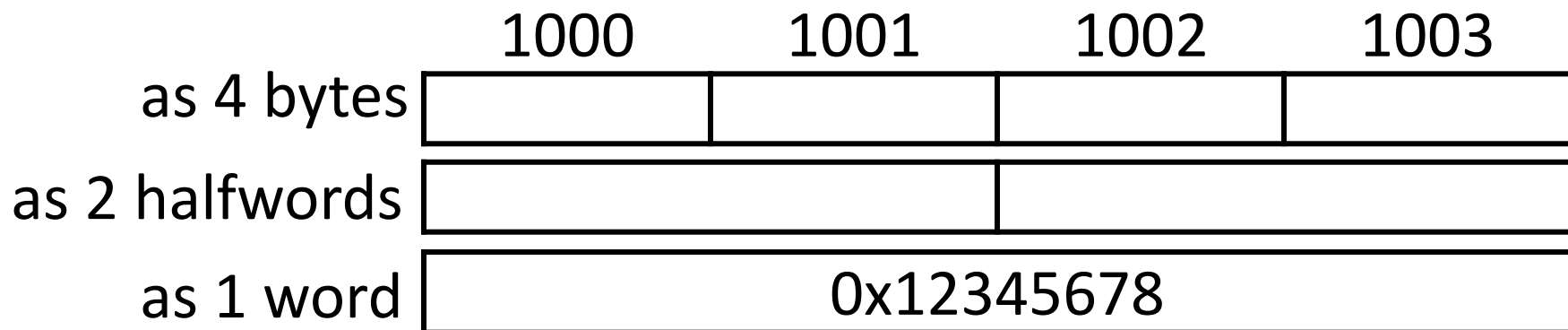Big Endian = most significant part first (MIPS, networks)



Memory Layout

Examples (big/little endian):

r5 contains 5 (0x00000005)


SB r5, 2(r0)

LB r6, 2(r0)

SW r5, 8(r0)

LB r7, 8(r0)

LB r8, 11(r0)

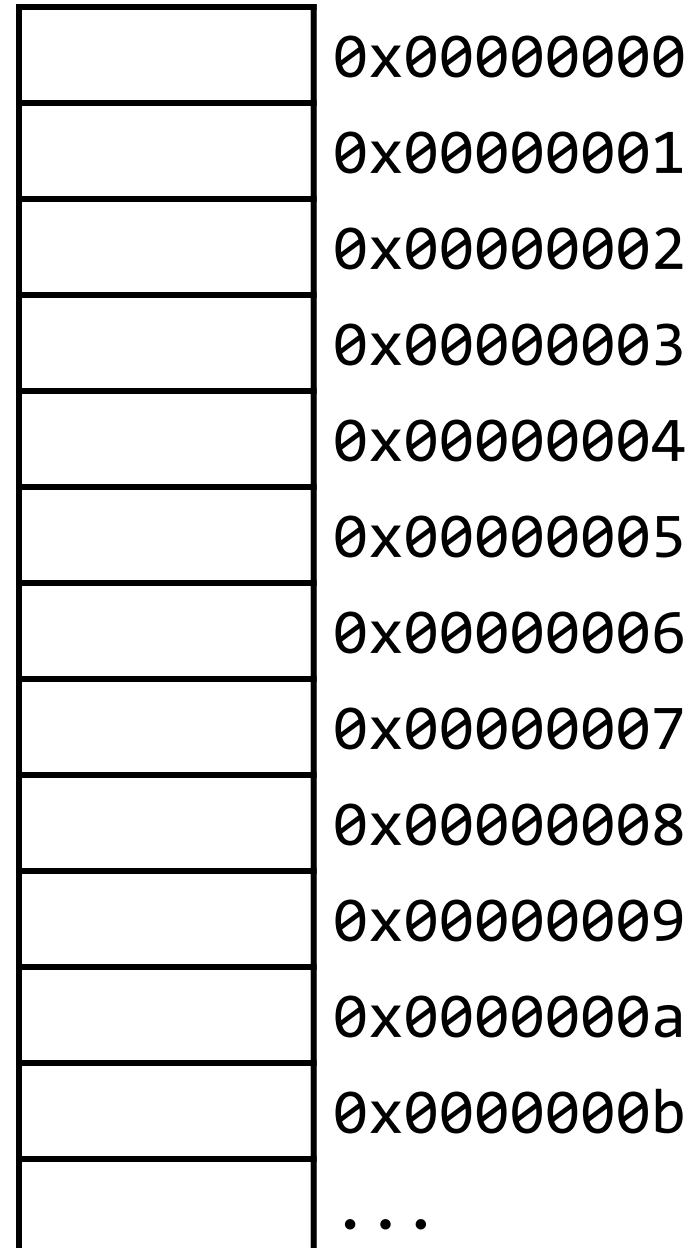

MIPS Instruction Types

Arithmetic/Logical

- R-type: result and two source registers, shift amount
- I-type: 16-bit immediate with sign/zero extension

Memory Access

- load/store between registers and memory
- word, half-word and byte operations

Control flow

- conditional branches: pc-relative addresses
- jumps: fixed offsets, register absolute

Control Flow: Absolute Jump

00001001000000000000000000000000000001


op
6 bits

immediate
26 bits

J-Type

op	Mnemonic	Description
0x2	J target	$PC = (PC+4)_{31..28} \cdot \text{target} \cdot 00$

Absolute Jump

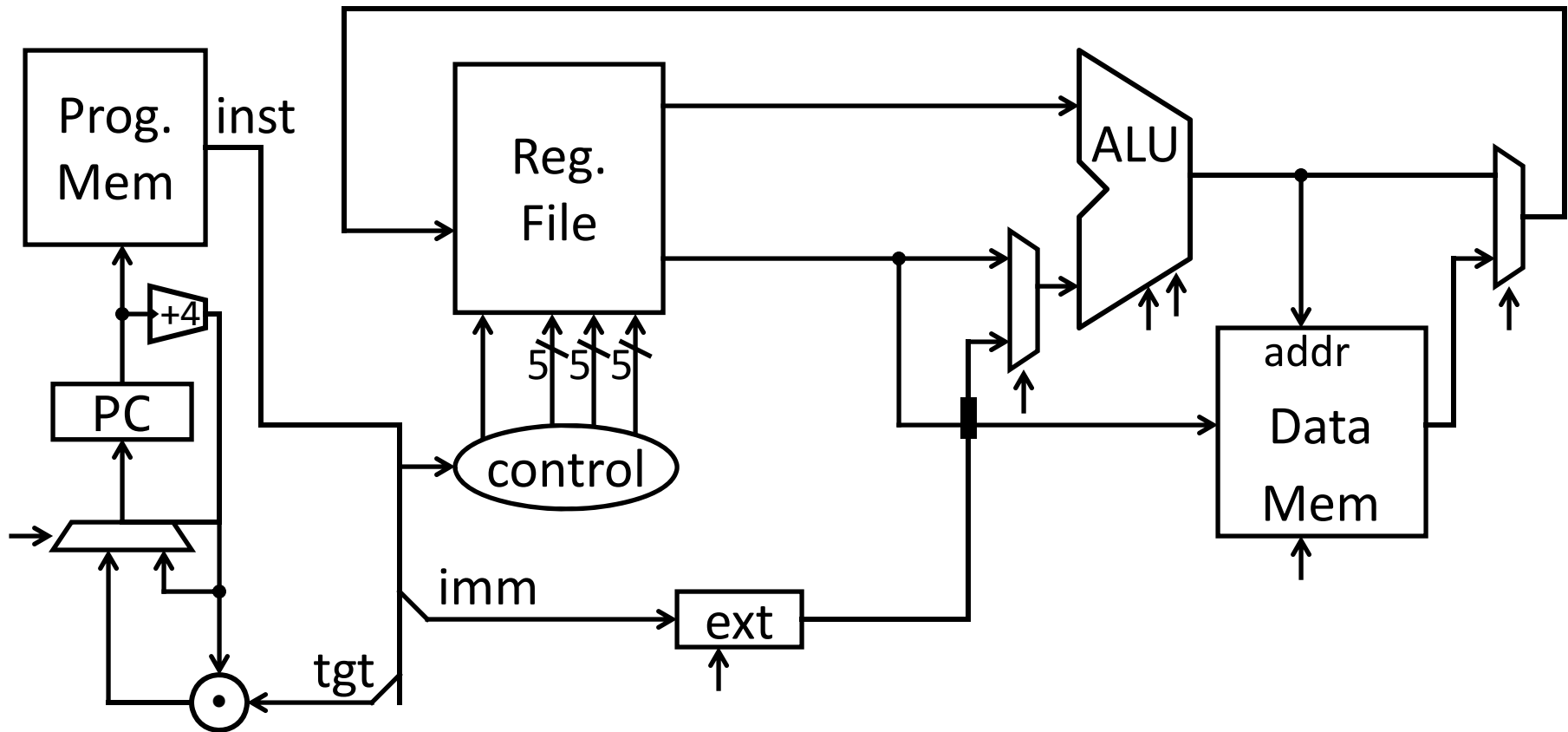

Control Flow: Jump Register


000000000110000000000000000000001000

op rs - - - func
6 bits 5 bits 5 bits 5 bits 5 bits 6 bits

R-Type

op	func	mnemonic	description
0x0	0x08	JR rs	PC = R[rs]

Jump Register

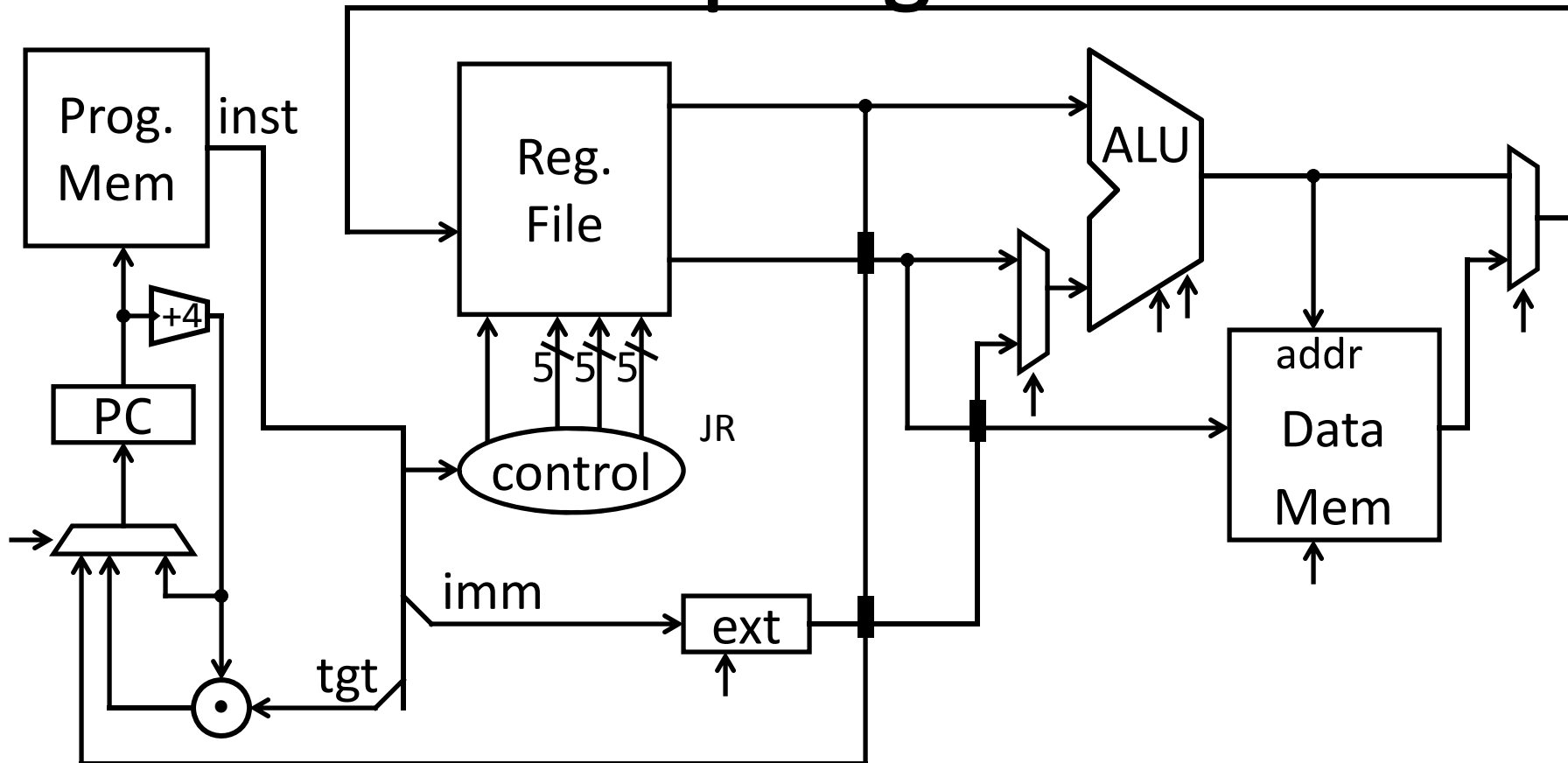

Examples

E.g. Use Jump or Jump Register instruction to jump to 0xabcd1234

But, what about a jump based on a condition?

assume $0 \leq r3 \leq 1$

if ($r3 == 0$) jump to 0xdecafe00

else jump to 0xabcd1234

Control Flow: Branches

0001000010100001000000000000000011



op

rs

rd

offset

6 bits

5 bits

5 bits

16 bits


I-Type

signed offsets

op	mnemonic	description
0x4	BEQ rs, rd, offset	if R[rs] == R[rd] then PC = PC+4 + (offset<<2)
0x5	BNE rs, rd, offset	if R[rs] != R[rd] then PC = PC+4 + (offset<<2)



Control Flow: Branches

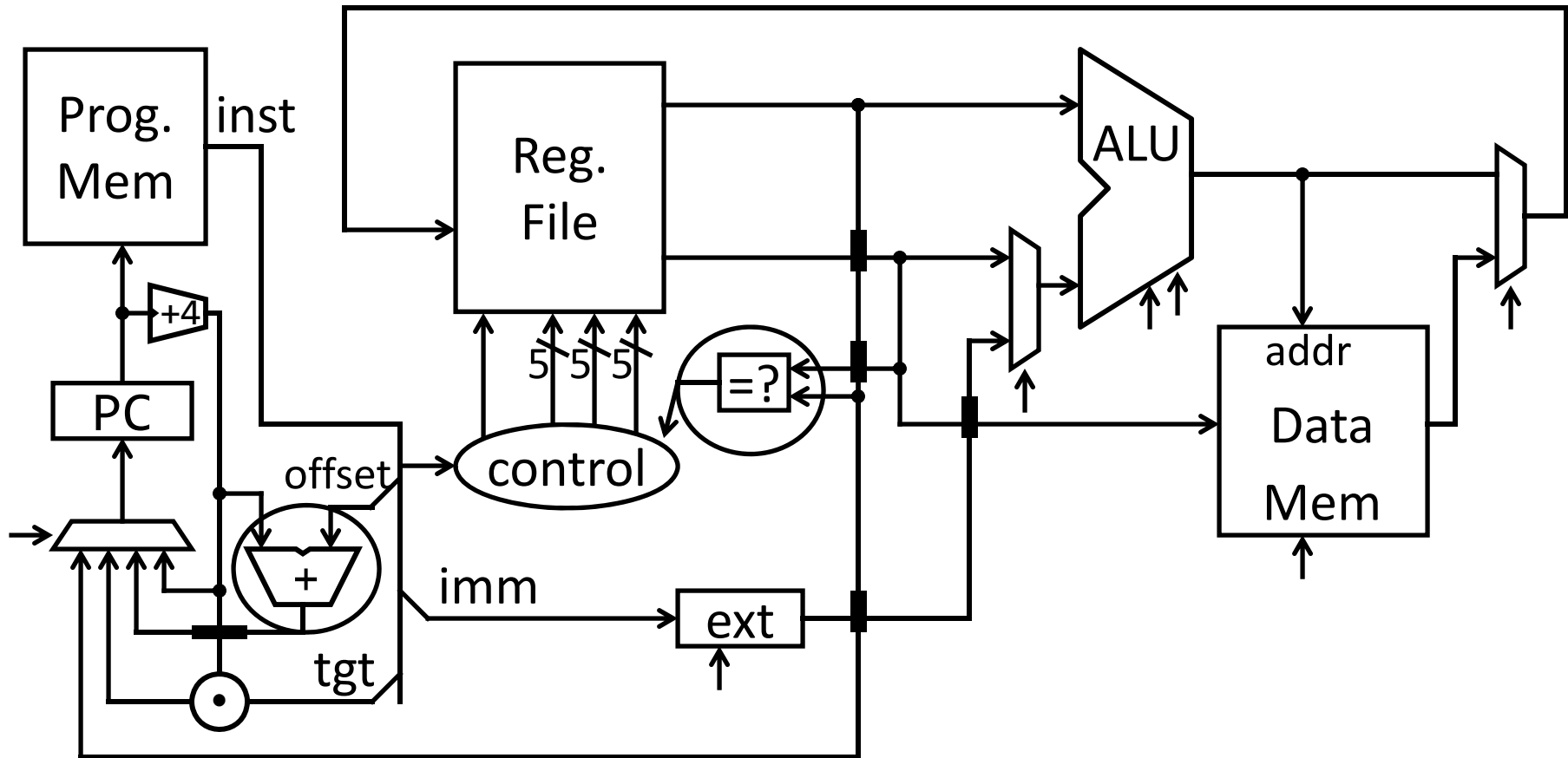

Control Flow: More Branches

Conditional Jumps (cont.)

00000100101000010000000000000010

op rs subop offset
 6 bits 5 bits 5 bits 16 bits


almost I-Type

signed offsets

op	subop	mnemonic	description
0x1	0x0	BLTZ rs, offset	if $R[rs] < 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x1	0x1	BGEZ rs, offset	if $R[rs] \geq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x6	0x0	BLEZ rs, offset	if $R[rs] \leq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x7	0x0	BGTZ rs, offset	if $R[rs] > 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$



Control Flow: More Branches

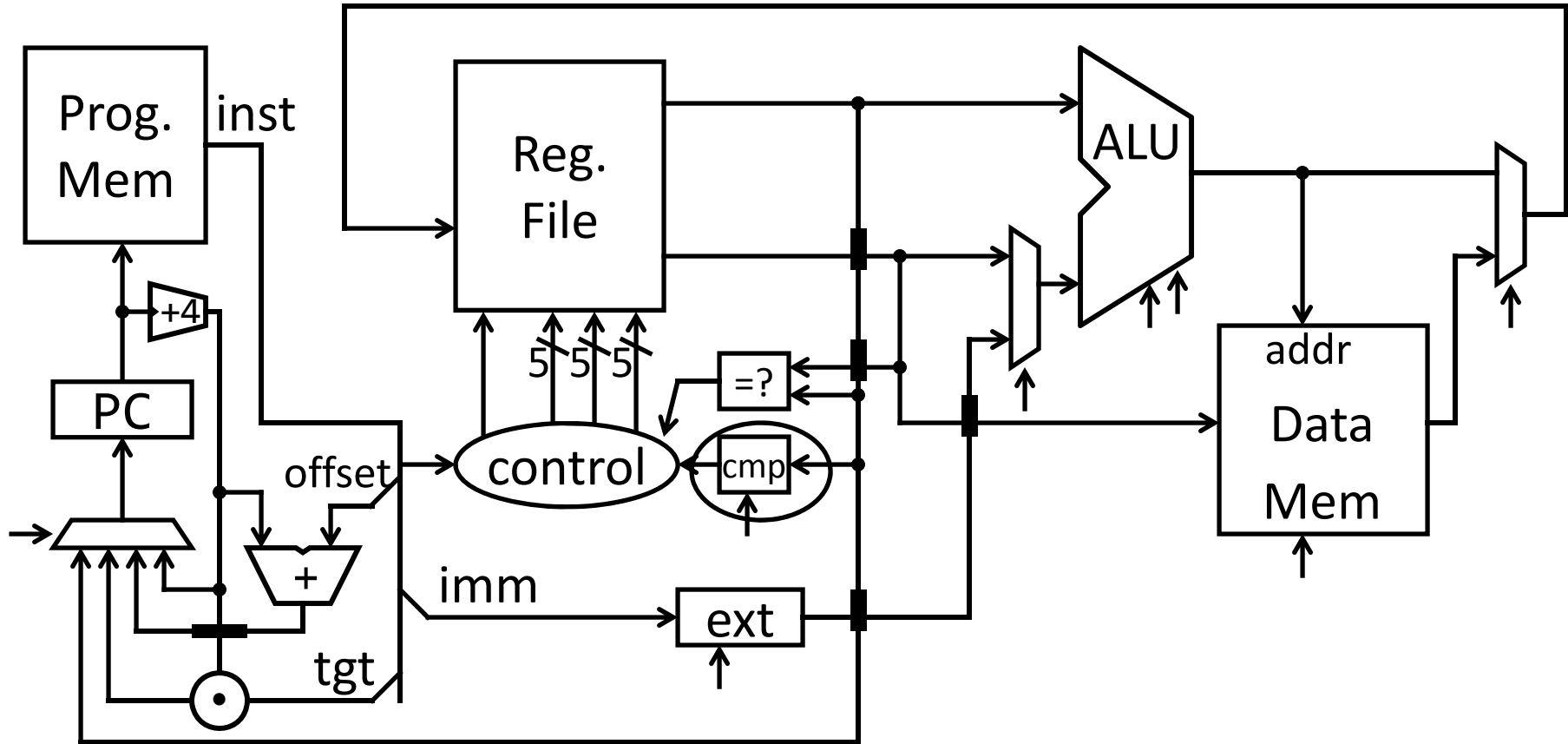

Control Flow: Jump and Link

Why? Function/procedure calls

00001101000000000000000000000001



op

immediate

6 bits


26 bits

J-Type

Discuss later

op	mnemonic	description
0x3	JAL target	r31 = PC+8 (+8 due to branch delay slot) PC = (PC+4) _{31..28} • target • 00

Jump and Link

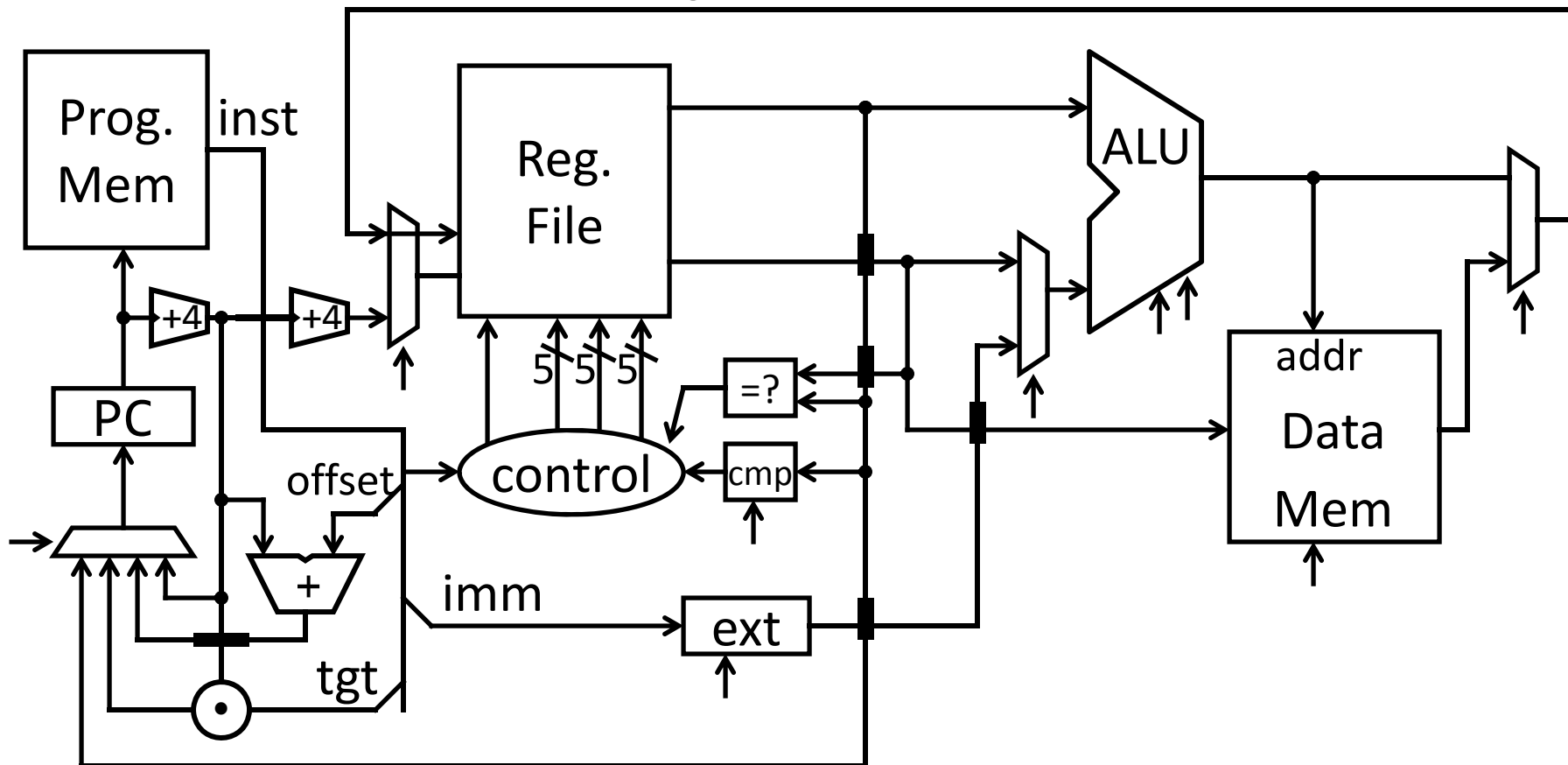

Goals for today

MIPS Datapath

- Memory layout
- Control Instructions

Performance

- How to get it?
- CPI (Cycles Per Instruction)
- MIPS (Instructions Per Cycle)
- Clock Frequency

Pipelining

- Latency vs throughput

Questions

How do we measure performance?

What is the performance of a single cycle CPU?

How do I get performance?

See: P&H 1.6

Performance

How do I get it?


Parallelism

Pipelining


Both!

Performance: Aside

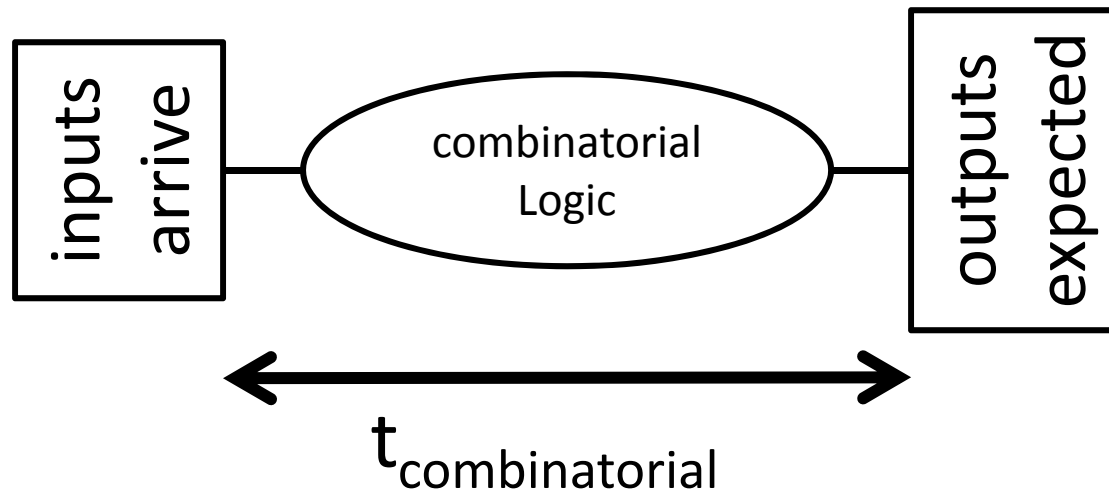Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



4-bit Ripple Carry Adder

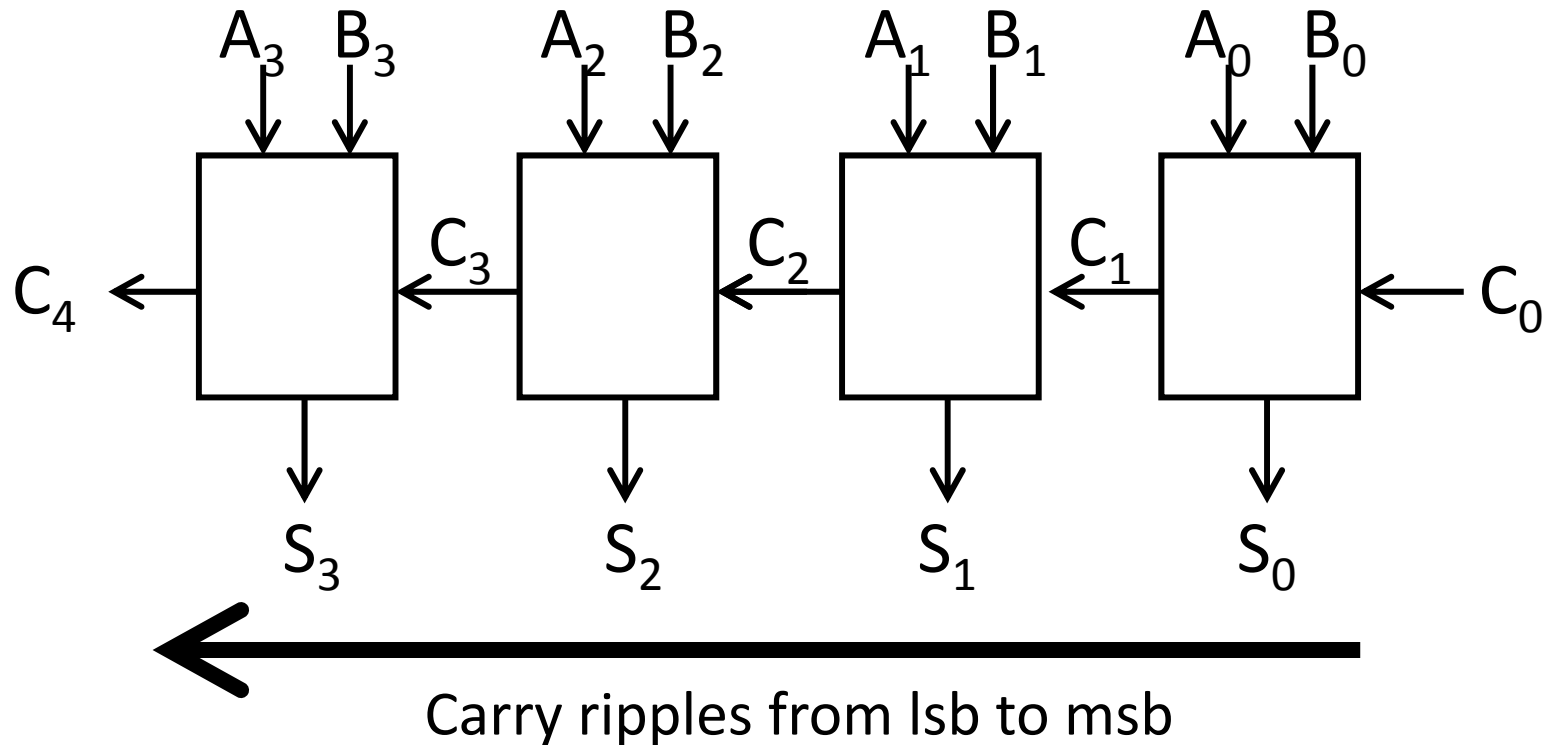

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...

Adding

Main ALU, slows us down

Does it need to be this slow?

Observations

- Have to wait for C_{in}
- Can we compute in parallel in some way?
- CLA carry look-ahead adder

Carry Look Ahead Logic


Can we reason C_{out} independent of C_{in} ?

- *Just based on (A,B) only*

When is $C_{out} == 1$, irrespective of C_{in} ?

If $C_{in} == 1$, when is C_{out} also $== 1$

1-bit Adder with Carry

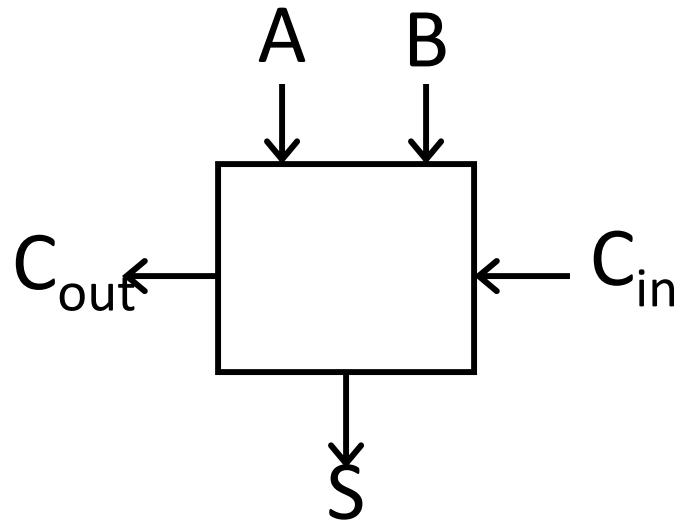


Full Addder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

1-bit CLA adder

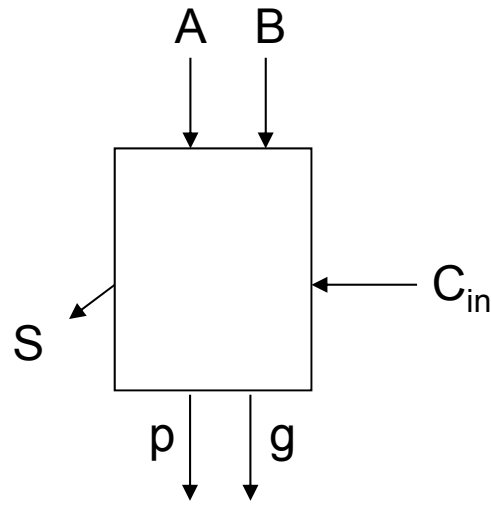

Create two terms: ***propagator, generator***

$g = 1$, *generates* C_{out} : $g = AB$


- Irrespective of C_{in}

$p = 1$, *propagates* C_{in} to C_{out} : $p = A + B$

p and g generated in 1 gate delay

S is 2 gate delay ***after*** we get C_{in}

4-bit CLA

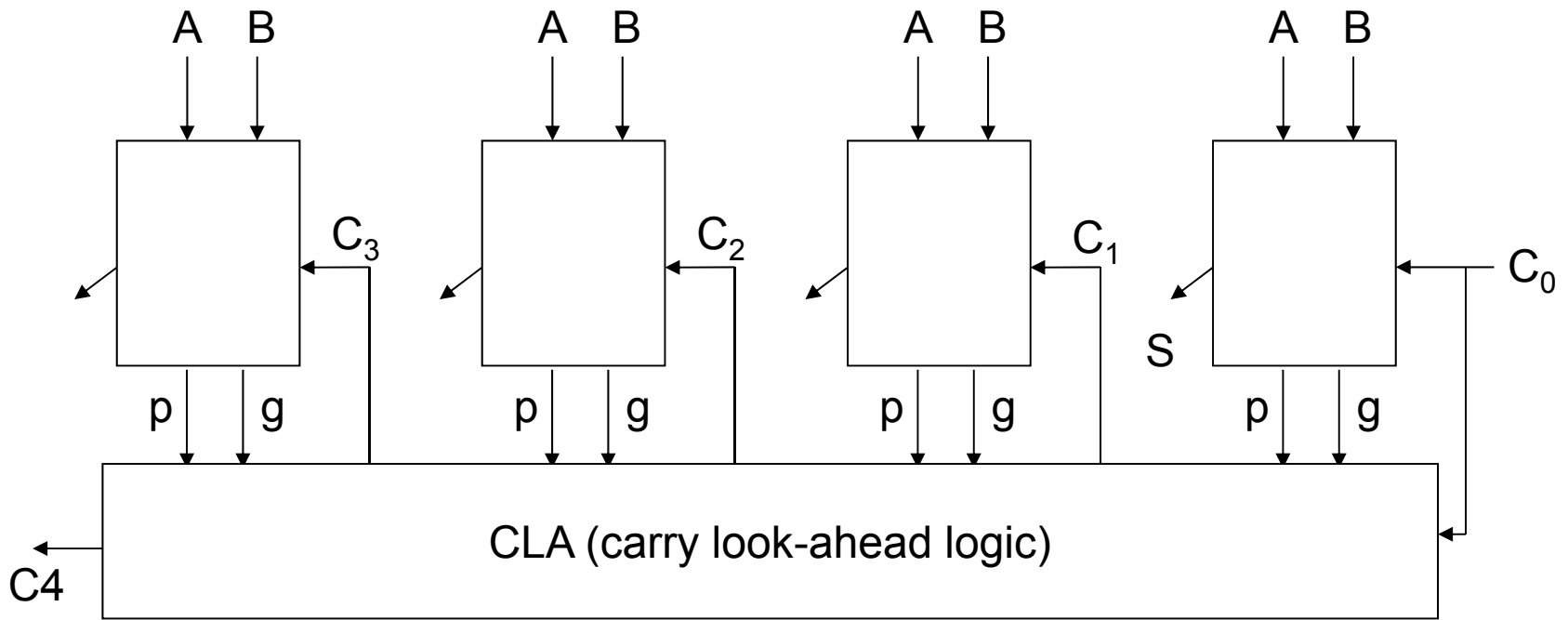

Performance

How do I get it?

Parallelism

Pipelining

Both!

Goals for today

MIPS Datapath

- Memory layout
- Control Instructions

Performance

- How to get it? Parallelism and Pipeline!

- CPI (Cycles Per Instruction)
- MIPS (Instructions Per Cycle)
- Clock Frequency

Next Time

Pipelining

- Latency vs throughput