Numbers & Arithmetic

Hakim Weatherspoon
CS 3410, Spring 2011
Computer Science
Cornell University

See: P&H Chapter 2.4 - 2.6, 3.2, C.5 – C.6

Announcements

Make sure you are

- Registered for class
- Can access CMS
- Have a Section you can go to
- Have a project partner

Sections are on this week

HW 1 out later today

- Due in one week, start early
- Work alone
- Use your resources
  - Class notes, book, Sections, office hours, newsgroup, CSUGLab

Announcements

Check online syllabus/schedule

- Slides and Reading for lectures
- Office Hours
- Homework and Programming Assignments
- Prelims: Thursday, March 11 and April 28th

- Schedule is subject to change

Goals for today

Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Subtraction (two's compliment)
- Performance

Logic Minimization

- How to implement a desired function?

a	b	c	out
0	**0**	**0**	**0**
0	**0**	**1**	**1**
0	**1**	**0**	**0**
0	**1**	**1**	**1**
1	**0**	**0**	**0**
1	**0**	**1**	**1**
1	**1**	**0**	**0**
1	**1**	**1**	**0**

Logic Minimization

- How to implement a desired function?

a	b	c	out	minterm
0	**0**	**0**	**0**	$\bar{a}\,\bar{b}\,\bar{c}$
0	**0**	**1**	**1**	$\bar{a}\,\bar{b}\,c$
0	**1**	**0**	**0**	$\bar{a}\,b\,\bar{c}$
0	**1**	**1**	**1**	$\bar{a}\,b\,c$
1	**0**	**0**	**0**	$a\,\bar{b}\,\bar{c}$
1	**0**	**1**	**1**	$a\,\bar{b}\,c$
1	**1**	**0**	**0**	$a\,b\,\bar{c}$
1	**1**	**1**	**0**	$a\,b\,c$

sum of products:

- OR of all minterms where out=1

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

Karnaugh Maps

How does one find the most efficient equation?

- Manipulate algebraically until…?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits

- Decomposition & reuse of building blocks

Voting machine

- Voting Machine!
  - optical scan (thanks FL)

- Assume:
  - vote is recorded on paper by filling a circle
  - fixed number of choices
  - don't worry about "invalids"

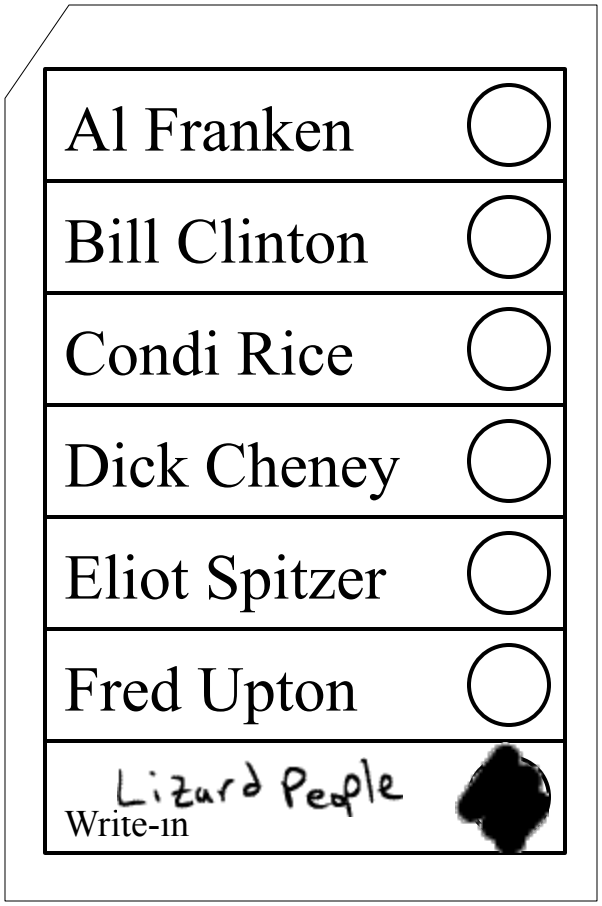

Voting Machine Components

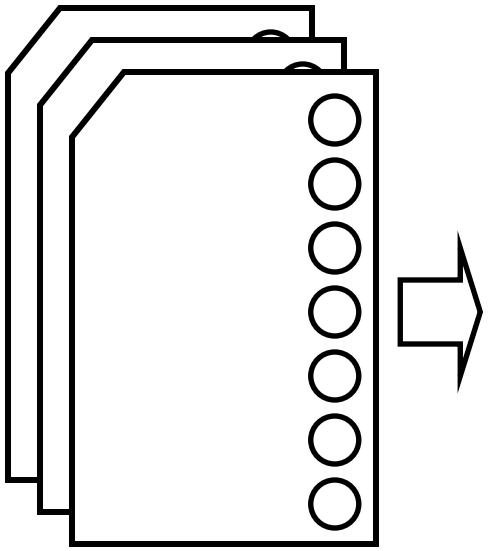

Ballots

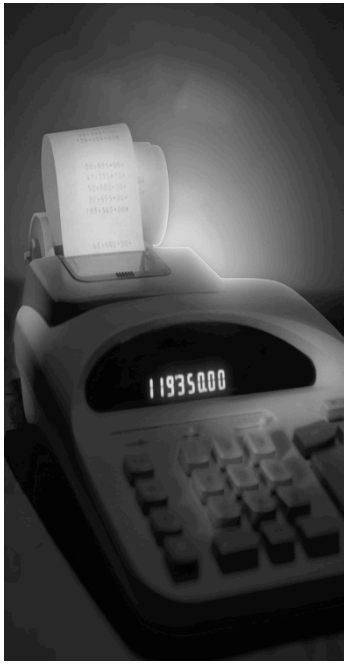

The 3410 optical scan vote ~~counter~~ reader machine

5 Essential Components?

- Input: paper with at exactly one mark
- Datapath: process current ballot
- Output: a number the supervisor can record
- Memory & control: none for now

Input

- Photo-sensitive transistor
  - photons replenish gate depletion region
  - can distinguish dark and light spots on paper

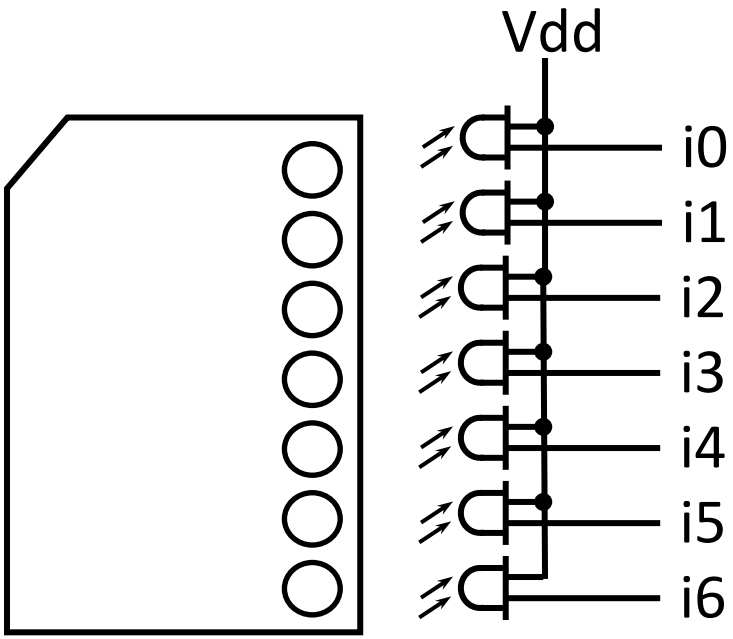

- Use array of N sensors for voting machine input

Output

- 7-Segment LED
  - photons emitted when electrons fall into holes

Block Diagram

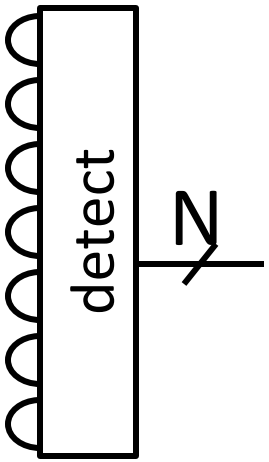

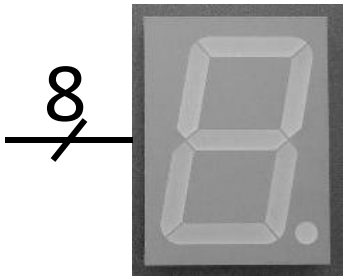

Encoders

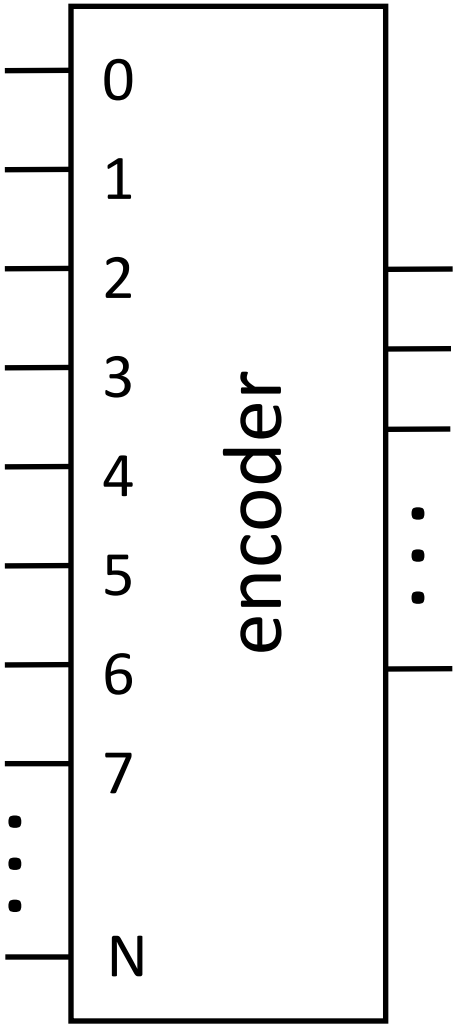

- N might be large
- Routing wires is expensive

- More efficient encoding?

Number Representations

- Base 10 - Decimal

$$\underline{6}\ \underline{3}\ \underline{7}$$

$$10^2\ 10^1\ 10^0$$

- Just as easily use other bases
  - Base 2 - Binary
  - Base 8 - Octal
  - Base 16 - Hexadecimal

Counting

- Counting

Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

Hexadecimal, Binary, Octal Conversions

Encoder Implementation

- Implementation . . .
  - assume 8 choices, exactly one mark detected

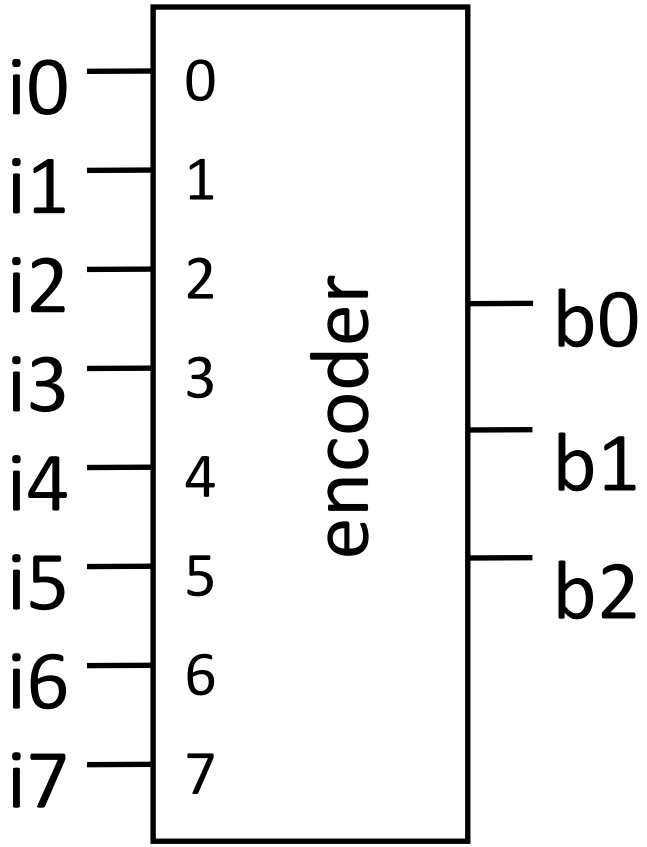

3-bit encoder

(8-to-3)

Ballot Reading

7-Segment LED Decoder

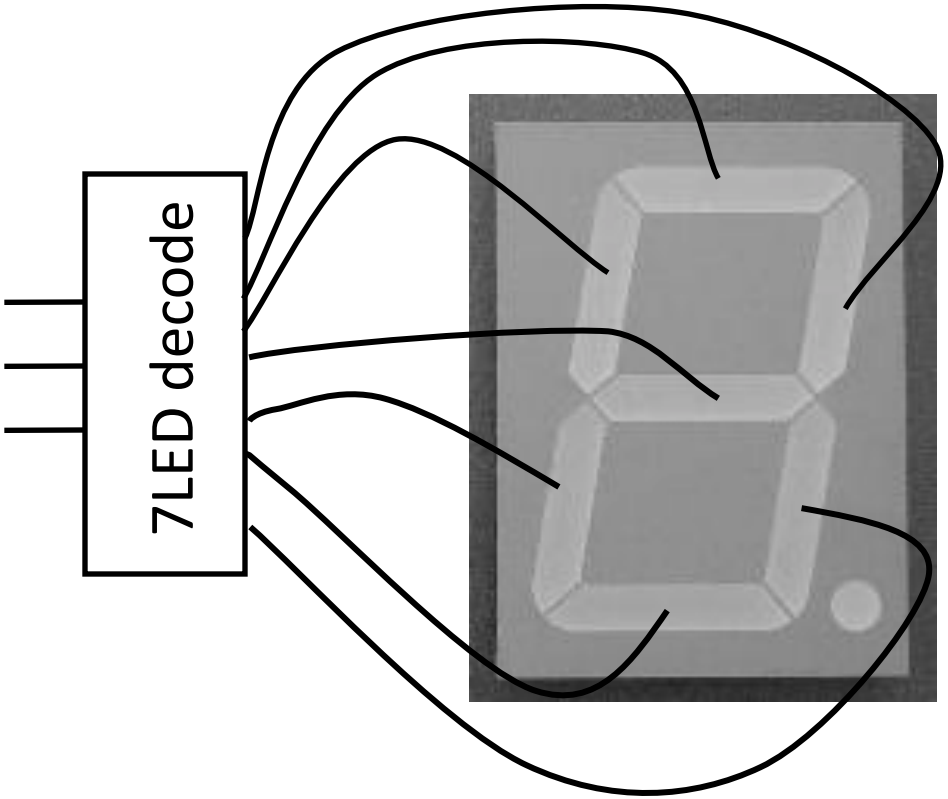

- 3 inputs
- encode 0 – 7 in binary

- 7 outputs
- one for each LED

7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							

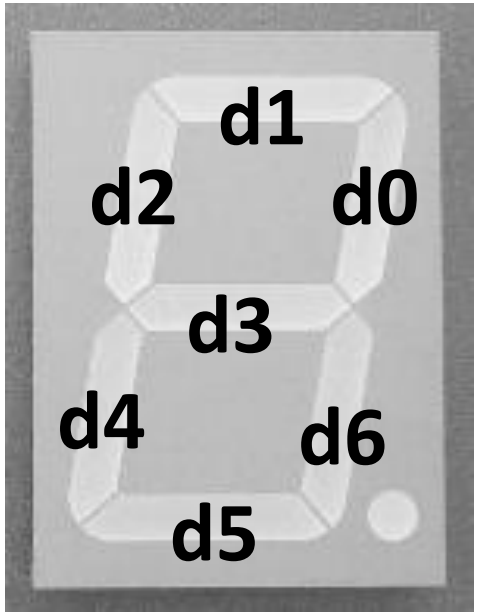

7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

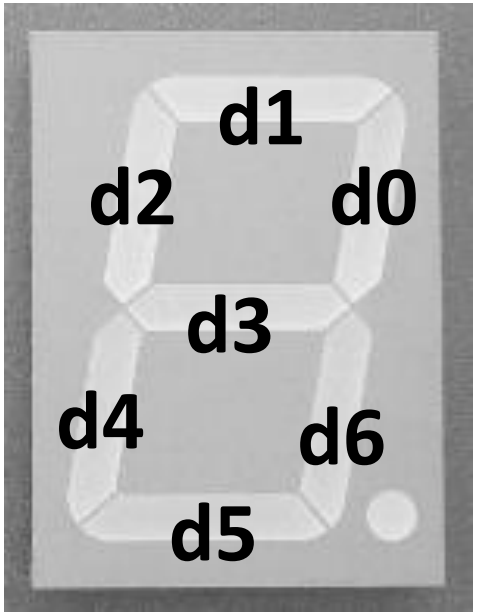

Ballot Reading and Display

Building Blocks

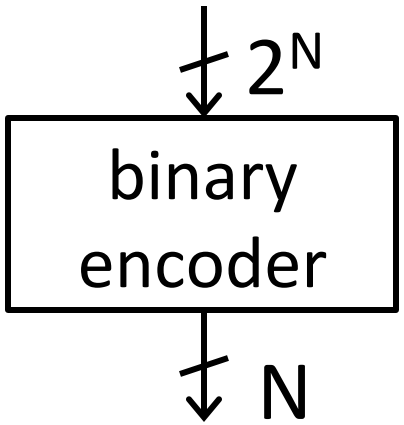

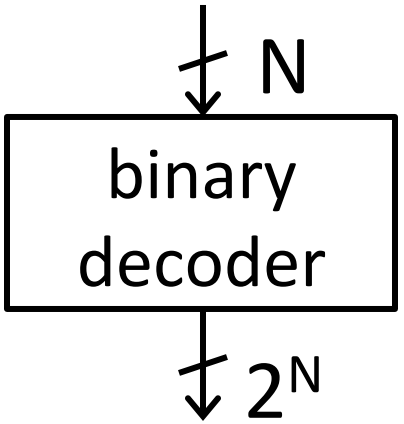

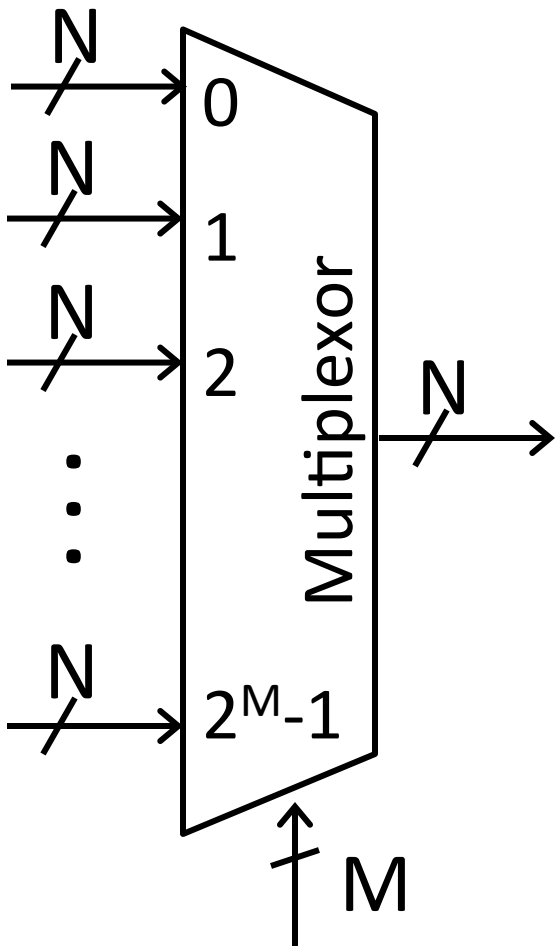

Goals for today

Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Subtraction (two's compliment)
- Performance

Binary Addition

183
+ 254

- Addition works the same way regardless of base
  - Add the digits in each position
  - Propagate the carry

+ 011100

1-bit Adder

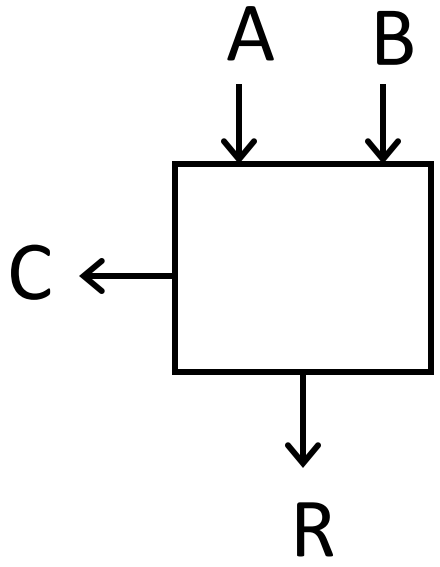

Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

1-bit Adder with Carry

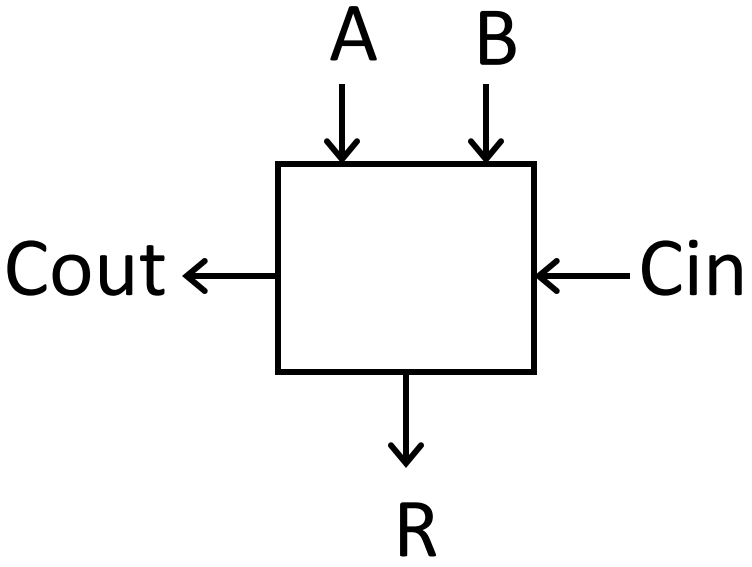

Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

4-bit Adder

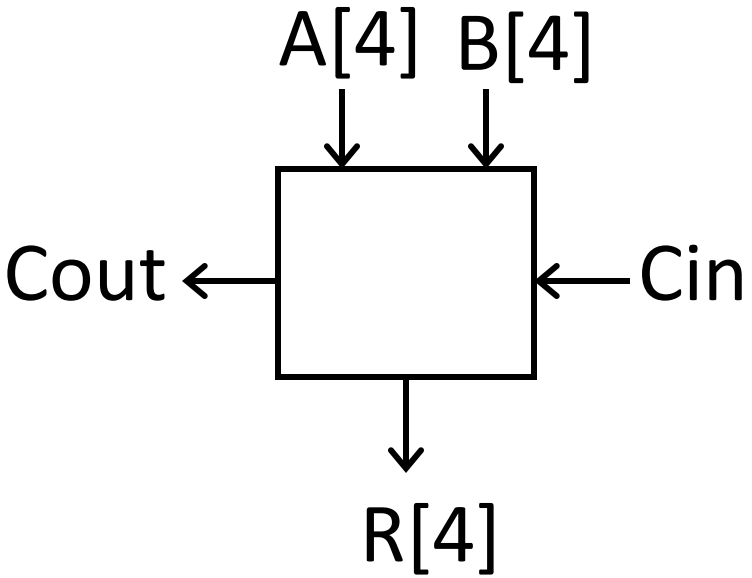

4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

4-bit Adder

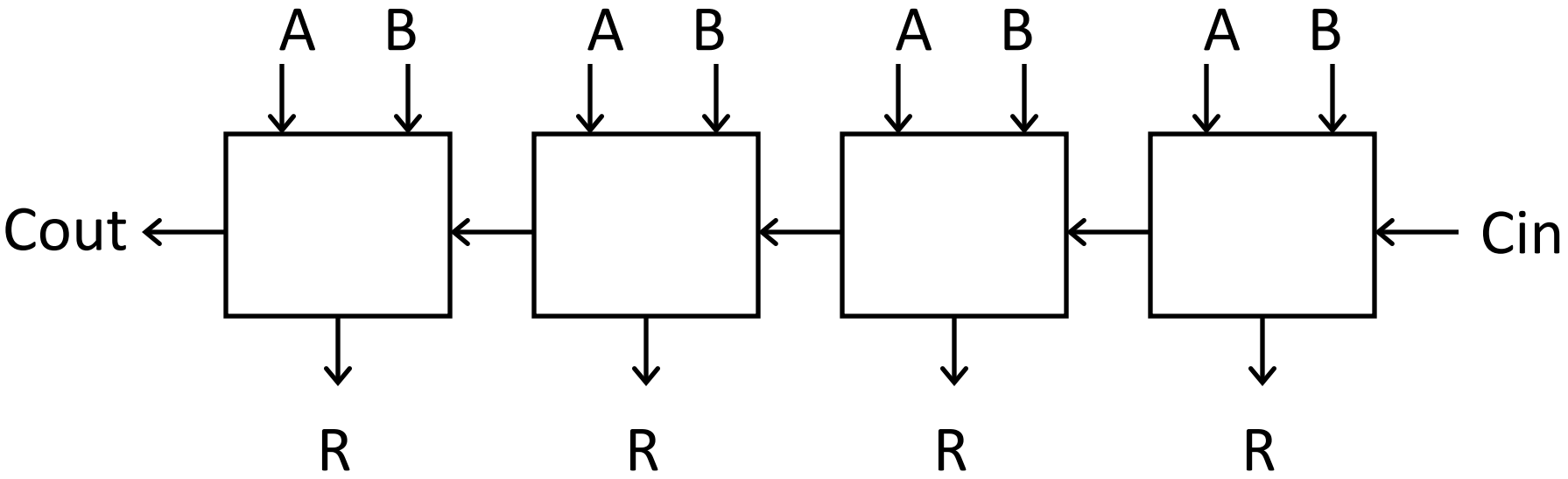

4-bit Adder

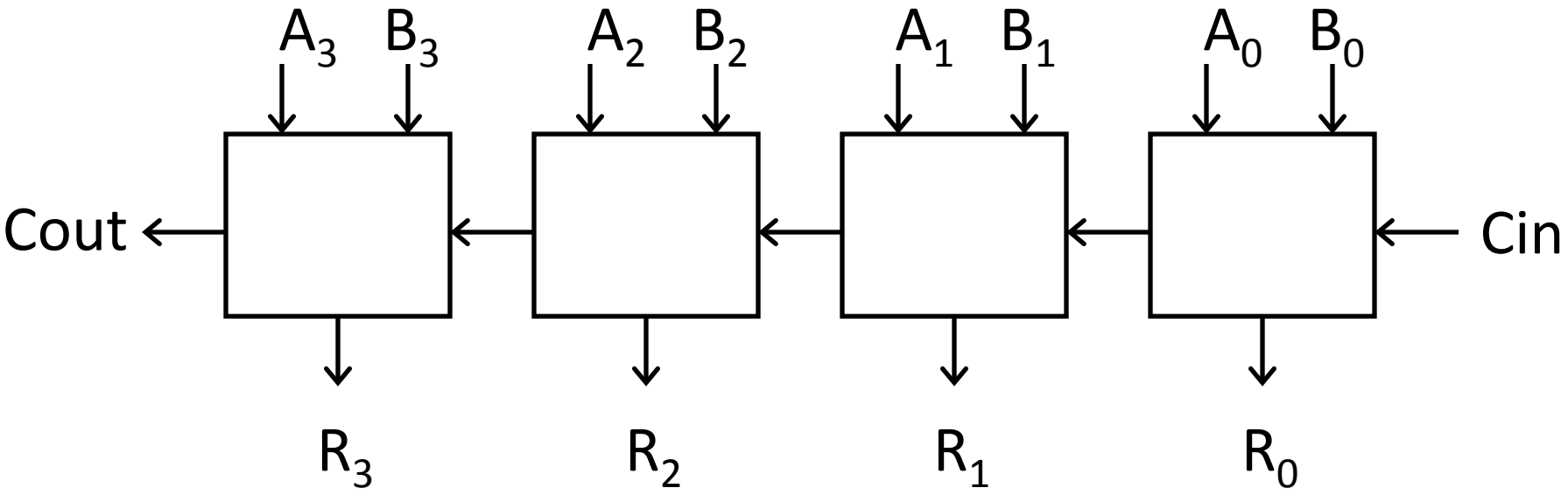

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out

Arithmetic with Negative Numbers

- Addition with negatives:
  - pos + pos add magnitudes, result positive
  - neg + neg add magnitudes, result negative
  - pos + neg subtract smaller magnitude, keep sign of bigger magnitude

First Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation
- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

Two's Complement Representation

- Better: Two's Complement Representation
- Leading 1's for negative numbers
- To negate any number:
  - complement *all* the bits
  - then add 1

Two's Complement

- Non-negatives Negatives
- (as usual): (two's complement: flip then add 1):
- +0 = 0000
- +1 = 0001 1110 -1 = 1111
- +2 = 0010 ~2 =
- +3 = 0011 ~3 = 1100 -3 = 1101
- +4 = 0100
- +5 = 0101
- +6 = 0110
- +7 = 0111 ~7 = 1000 -7 = 1001
- +8 = 1000 ~8 = 0111 -8 = 1000

Two's Complement Facts

- Signed two's complement
  - Negative numbers have leading 1's
  - zero is unique: +0 = - 0
  - wraps from largest positive to largest negative
- N bits can be used to represent
  - unsigned:
    - eg: 8 bits ⇒
  - signed (two's complement):
    - ex: 8 bits ⇒

Sign Extension & Truncation

- Extending to larger size

- Truncate to smaller size

Two's Complement Addition

- Addition with two's complement signed numbers
- Perform addition as usual, regardless of sign (it just works)

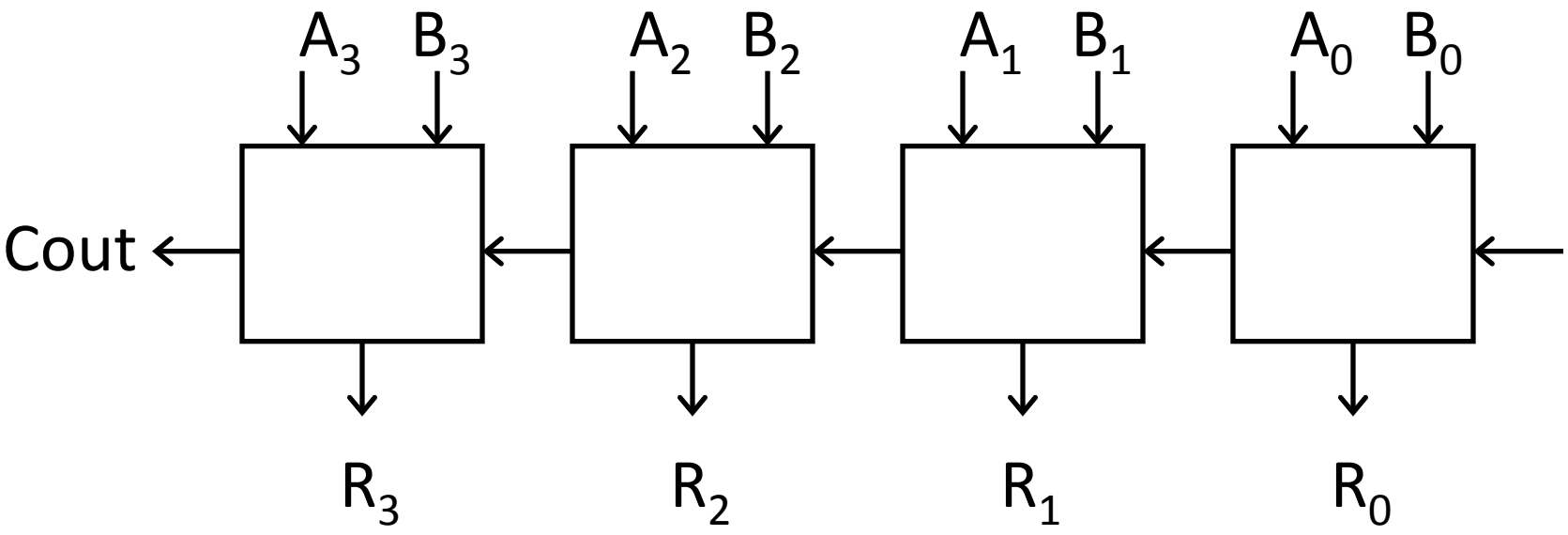

Diversion: 10's Complement

- How does that work?

$$\begin{array}{r} -154 \\ +283 \\ \hline \end{array}$$

Overflow

- Overflow
  - adding a negative and a positive?
  - adding two positives?
  - adding two negatives?
- Rule of thumb:
- Overflow happened iff
  carry into msb != carry out of msb

Two's Complement Adder

- Two's Complement Adder with overflow detection

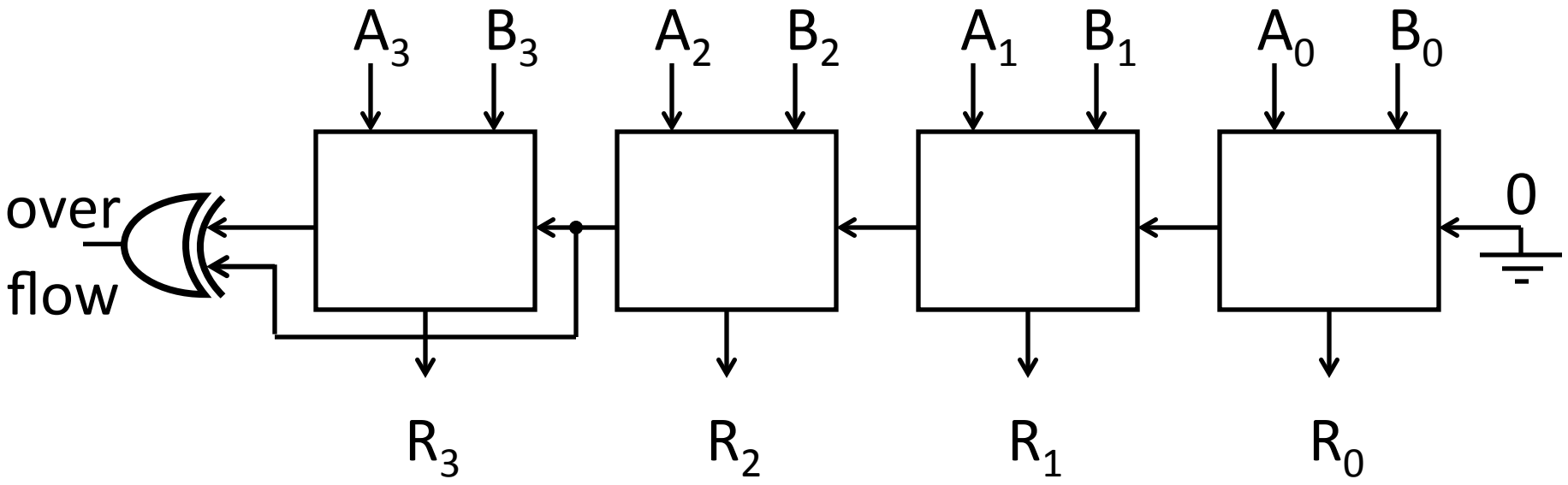

Binary Subtraction

- Two's Complement Subtraction
- Lazy approach –
- A – B = A + (-B) = A + (B + 1)

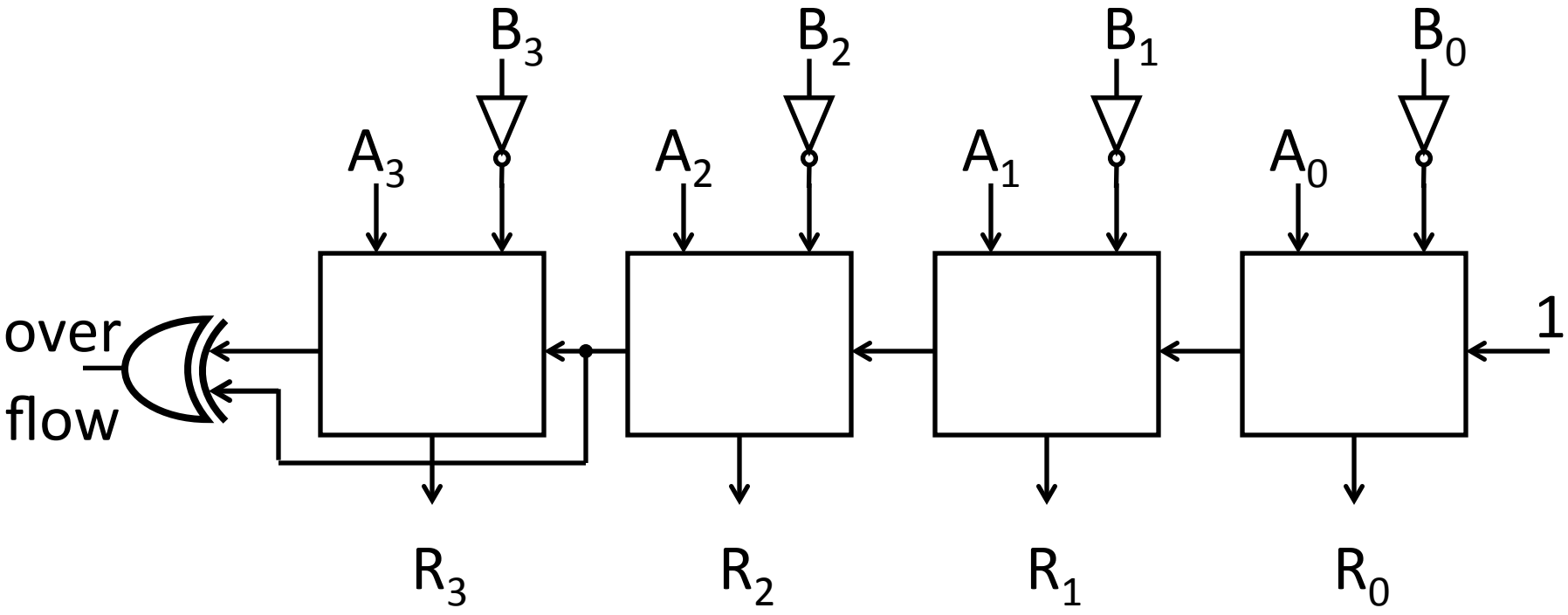

Q: What if (-B) overflows?

A Calculator

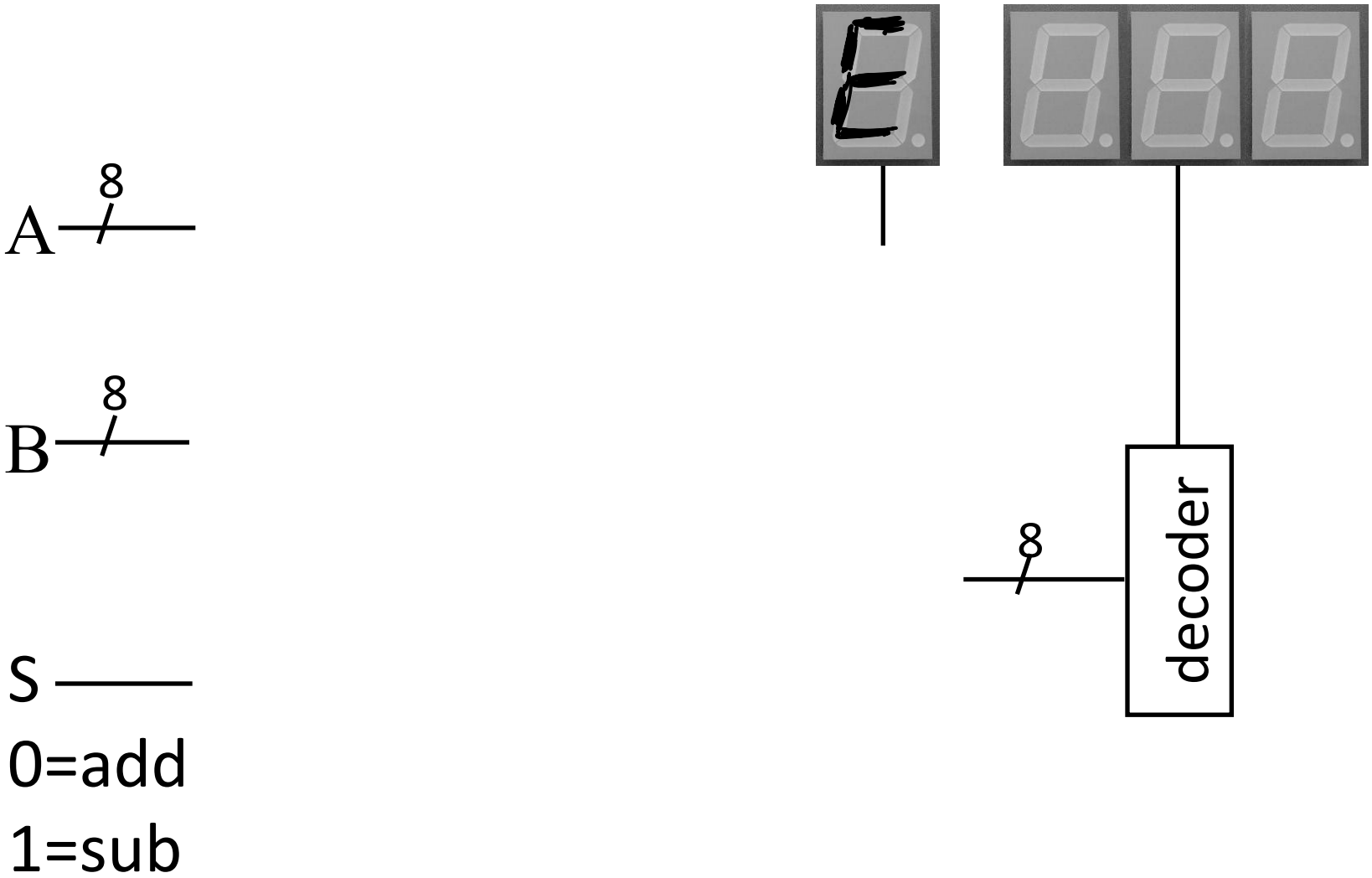

A Calculator

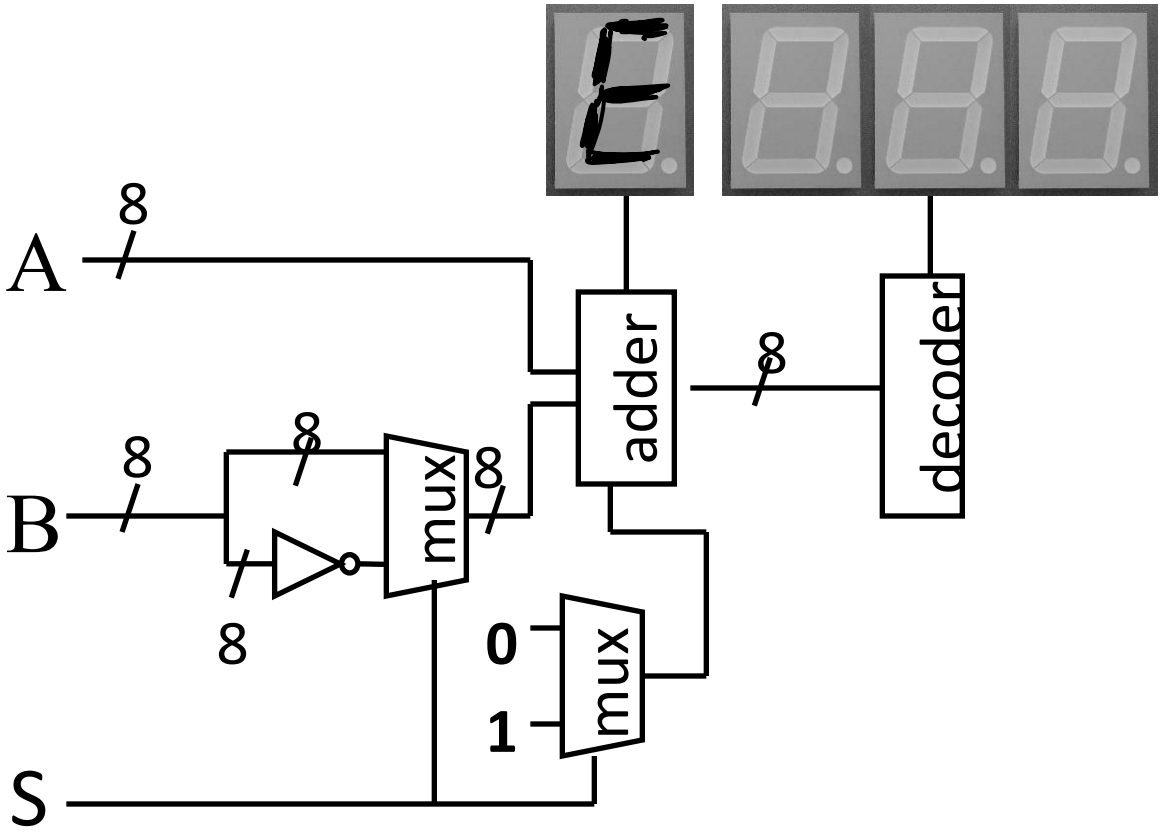

Efficiency and Generality

- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?

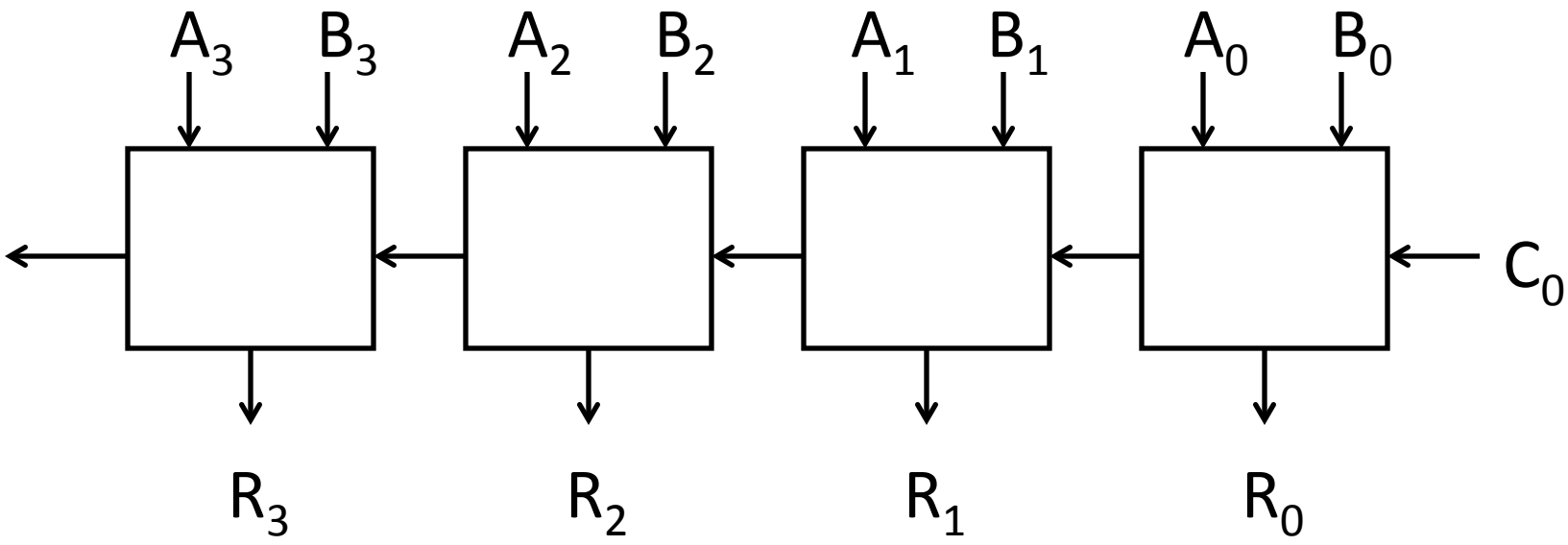

Performance

- Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)

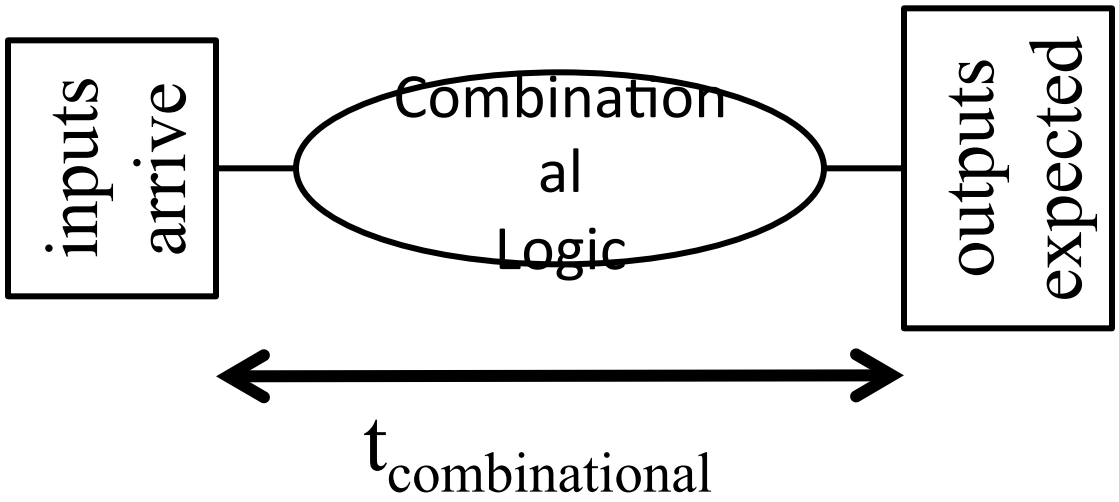

4-bit Ripple Carry Adder

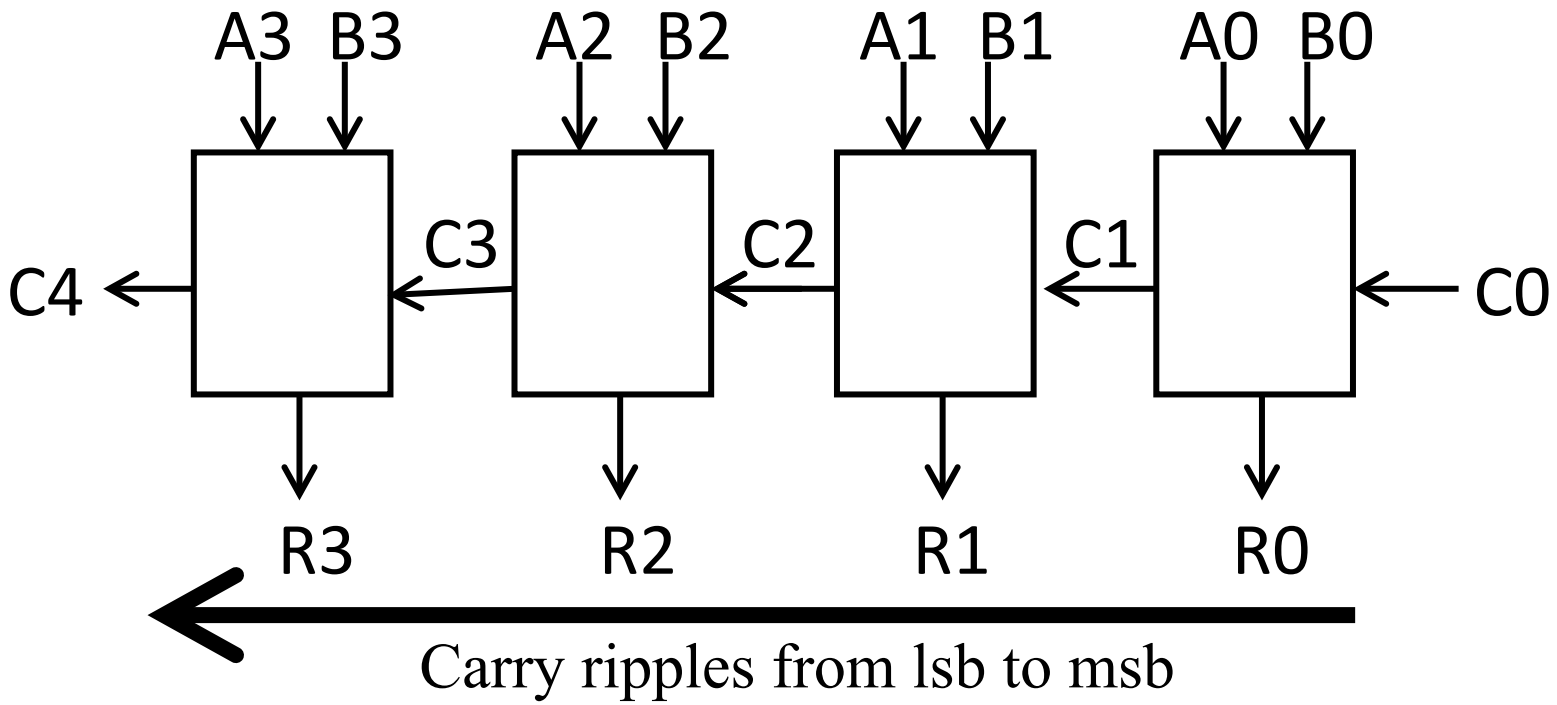

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- …

Summary

- We can now implement any combinational (combinatorial) logic circuit
  - Decompose large circuit into manageable blocks
    - Encoders, Decoders, Multiplexors, Adders, ...
  - Design each block
    - Binary encoded numbers for compactness
  - Can implement circuits using NAND or NOR gates
  - Can implement gates using use P- and N-transistors
  - And can add and subtract numbers (in two's compliment)!
  - Next time, state and finite state machines…